

Case study – Effect of utility-induced surges in a steel mill with variable speed drives

Edvard



Case study – Effect of utility-induced surges (A steel mill with variable speed drives); photo credit: dpncanada.com

Problem

A steel mill with variable speed drives (VSDs) had problems of frequent tripping of the VSDs with the indication '**overvoltage in AC line**'. Each tripping caused severe production disruption and resulted in considerable monetary loss due to lost production.

Steady-state measurements by true RMS voltmeter showed that voltage was normal and within the specified operating range of the VSD. A power line monitor was then used in the distribution board feeding the VSDs and the incoming power feeder to the mill. At both locations, the monitors showed **transient overvoltages** of damped oscillatory type waveform with an initial amplitude of **over 2.0 pu** and a **ringing frequency of about 700 Hz**.

The timing of disturbances coincided with the closing of capacitor banks in the utility substation feeding the steel mill (refer Figure 1a below).

Analysis

It was confirmed by the VSD manufacturer that the VSDs were provided with overvoltage protection set to operate at **1.6 pu voltage** for disturbances exceeding **40 μ s**.

Since the **switching transients** were above this protection threshold, the VSDs tripped.

It may be noted that switching on a bank of capacitors results in **high charging current inrush**. When this current passes through the line's inductance L , a momentary voltage surge occurs. Further interaction of the capacitor C with inductance L results in an oscillatory flow of current, which is damped by the resistance R in the system.

The oscillatory disturbance superimposed over the normal power-frequency voltage wave caused the overvoltage protection to operate.

Solution


The solution lies in reducing the transient peak to a value that is below the overvoltage protection threshold.

This was achieved in this case by installing a [surge protection device \(SPD\)](#) in each VSD. The SPD clamped the transient to a peak value of 1.5 pu thus avoiding the operation of overvoltage protection.

Another possible solution would have been **to install an inductor $L1$ in the switching circuit of the capacitor** for a few seconds and then shunt it by **switch S** .

Since the voltage seen by the incoming feeder to the mill would be the combination across C and $L1$, the transient will have a smaller amplitude. This solution will however call for cooperation from the utility as it involves additional equipment to be installed by them (*refer Figure 1b above*).

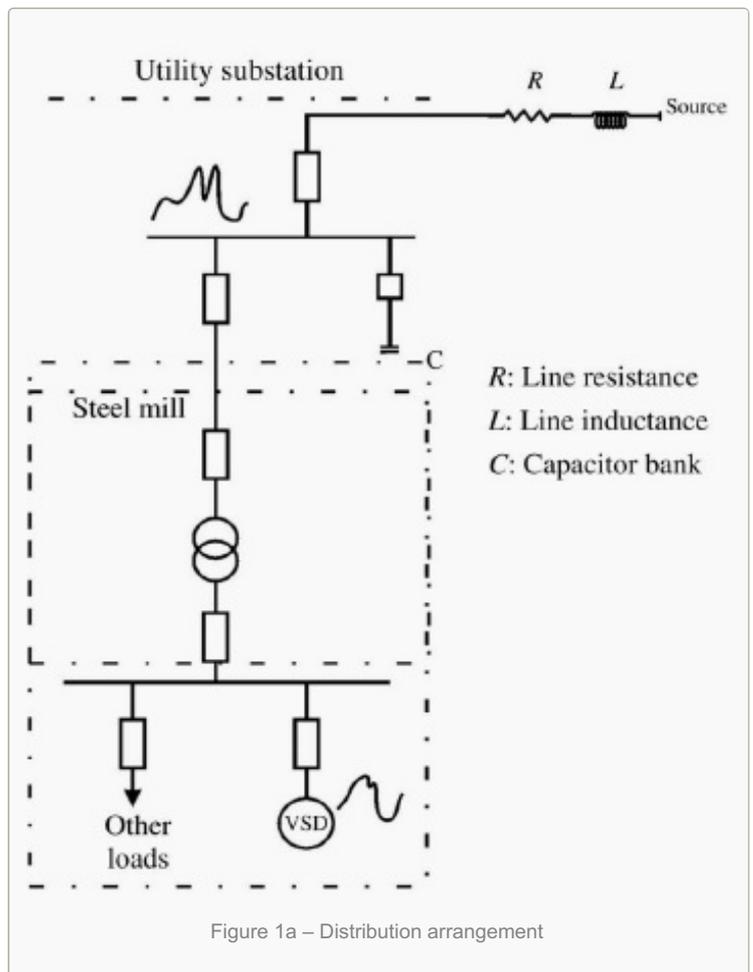Reference: *Practical Grounding, Bonding, Shielding and Surge Protection* – G. Vijayaraghavan, Mark Brown and Malcolm Barnes ([Get your harcopy from Amazon](#))



Source:

<http://electrical-engineering-portal.com/case-study-effect-of-utility-induced-surges>