

INTRODUCTION TO OHM'S LAW

What is Ohm's Law ?



In 1826 *Georg Simon Ohm* discovered that for metallic conductors there is substantially constant ratio of the potential difference between the ends of the conductor.

Ohm's Law states that the current flowing in an electric circuit is directly proportional to the applied voltage and inversely proportional to the resistance of the material.

$$I = \frac{V}{R}$$

Ohm's Law equation

I- current

V-voltage

R- resistance

Ohm's law is explained by the following statement.


1. Current varies directly with applied voltage

A change in the voltage applied to a circuit will cause the current flowing in the circuit to change. If the resistance is constant, the current change will follow the pattern of the voltage change. Doubling the potential difference doubles the current.

2. Current varies inversely with resistance

Changing the resistance in a circuit will also cause a change in current flow. If the voltage applied to a circuit is held constant, and the resistance in the circuit is increased. With more opposition to current flow in the circuit, the circuit current will decrease. On the other hand, if the resistance is decreased the amount of current flow in the circuit will be increased.

3. Voltage vs. current

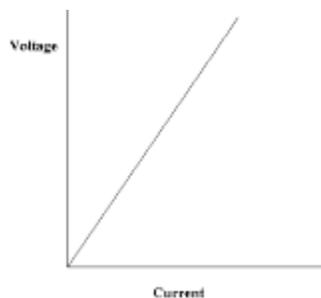


The relationship between voltage and current can be graphically represented with this illustration.

thus:

1. the higher the voltage, the larger the current
2. the higher the resistance the lower the current


AC Ohms Law

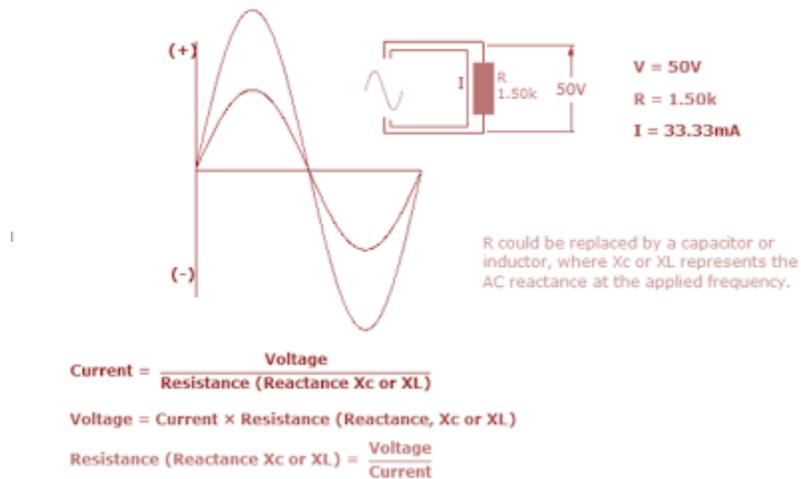

Ohms law can also be applied in *AC circuits*. But alternating voltage and currents are always changing. From zero, current and voltage builds up and reach its max peak in the positive value at 90 degrees and then back to zero and again to the negative peak value.

In this regard, Its only possible to calculate instantaneous values of voltage and current throughout its cycle.

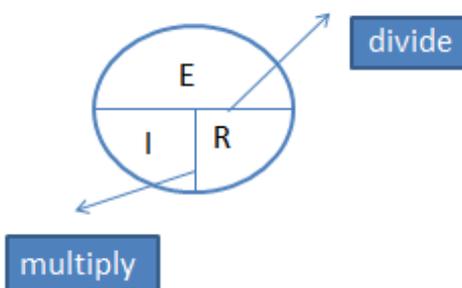For AC Ohms law can be expressed by the the same equation , where R could be replaced by a inductor or capacitor , where X_c or X_L is the AC *reactance*



Ohms Law Derived formulas formulas from
 Ohms law circle

$$V = I \times R$$

$$I = V / R$$

$$R = V / I$$

Source : <http://www.engineermaths.com/2010/11/introduction-to-ohms-law.html>