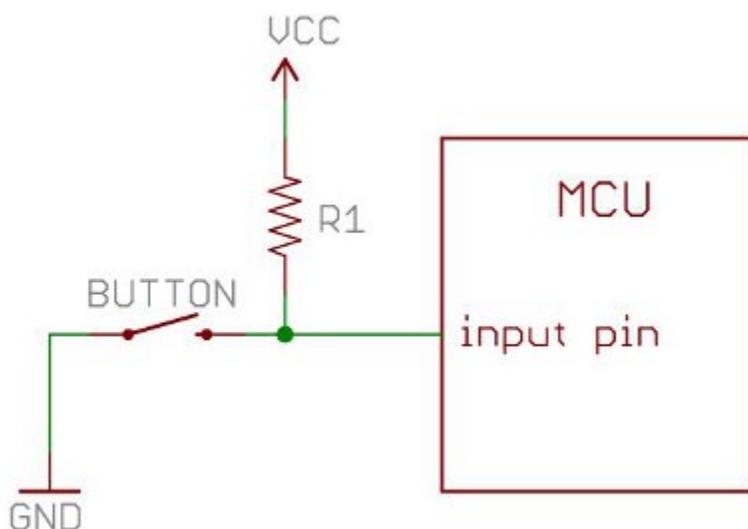


current they can withstand. Exceed a switch's maximum current rating, and you can expect melted plastic and magic smoke.

For example, this **SPDT slide switch** is great for controlling current flow in small projects (like **Simons** or **Metronomes**), but don't try using it to control beefy motor controllers, or strings of 100 LEDs. For that, consider using something like a **4A toggle switch** or a **6A lamp switch**.

User Input

Of course, user input is one of the more common applications for switches. For example, if you want to connect a switch to a microcontroller input pin, a simple circuit like this is all you'd need:



When the switch is open, the MCU pin is connected through the resistor to 5V. When the switch is closed, the pin is tied directly to GND. The resistor in that circuit is a **pull-up resistor**, required to bias the input high, and prevent a short to ground when the switch is closed.