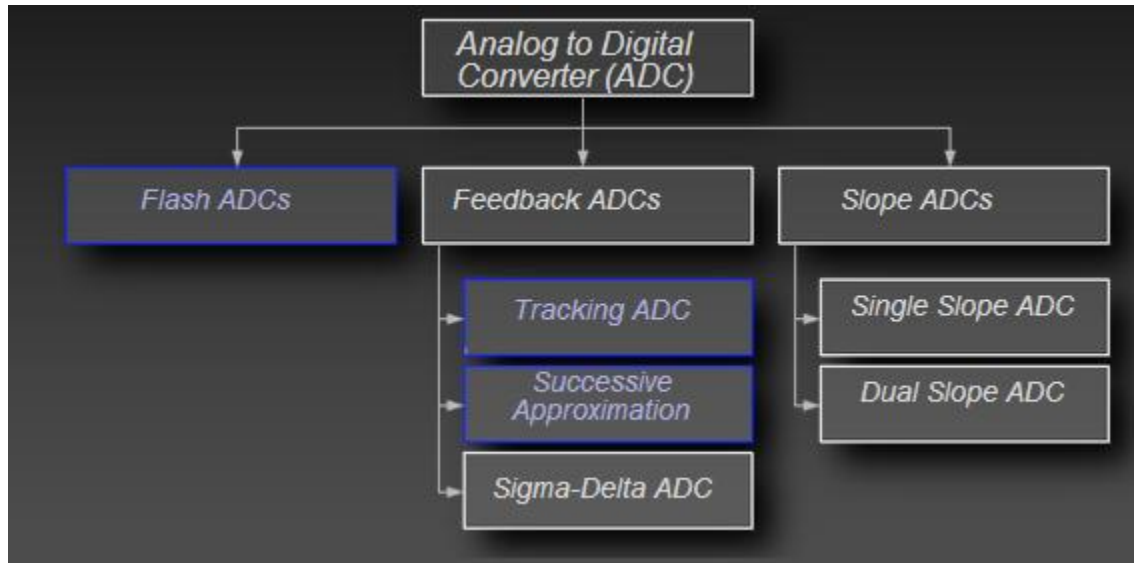


Analogue-to-Digital Converter

Analogue-to-Digital Converter don't operate continuously, but sample the analogue signal at diskrete intervals $T_s = 1/f_s$ and convert the sampled signal to digital form.



Nyquist-Shannon Sampling Theorem

When sampling a signal at discrete intervals the sampling frequency f_{max} must be greater than twice the highest frequency f_{max} of the input signal in order to be able to reconstruct the original perfectly from the sampled version.

The minimum sampling frequency f_s that allows reconstruction of the origin signal is known as the Nyquist frequency. Sampling at less than the Nyquist frequency causes aliasing.

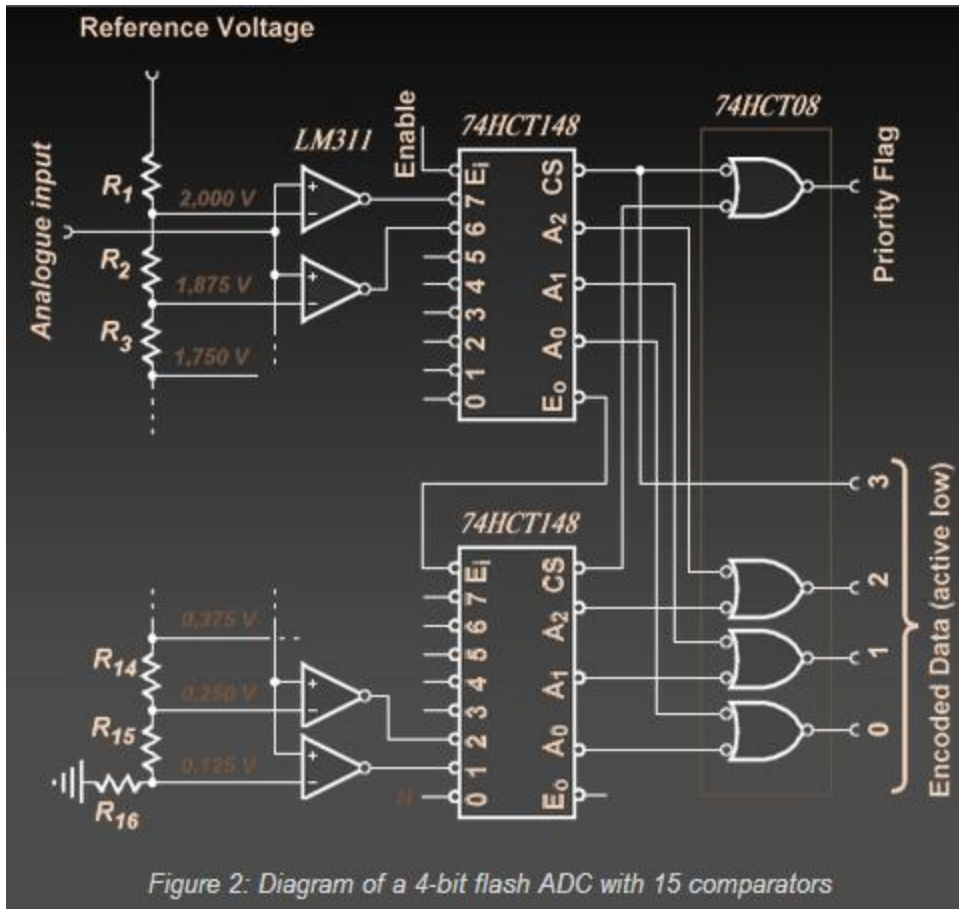


Figure 2: Diagram of a 4-bit flash ADC with 15 comparators

Flash ADC

Flash converters are so-called because they are the fastest type of ADC. Flash ADCs contain a chain of parallel comparators. They can be obtained with a limited precision only, are expensive and consume a considerable amount of power. The output of the comparators is converted to binary form by combinational logic (a priority encoder).

Flash ADCs perform $2^n - 1$ single-bit conversion in parallel. For the integrated ADC e.g. Maxim MAX104 with 8 Bit encoded data you need 255 comparators and it costs about 900 €. It has got a conversion time of 1 Nanosecond (1 Gsps).

Half-flash ADC

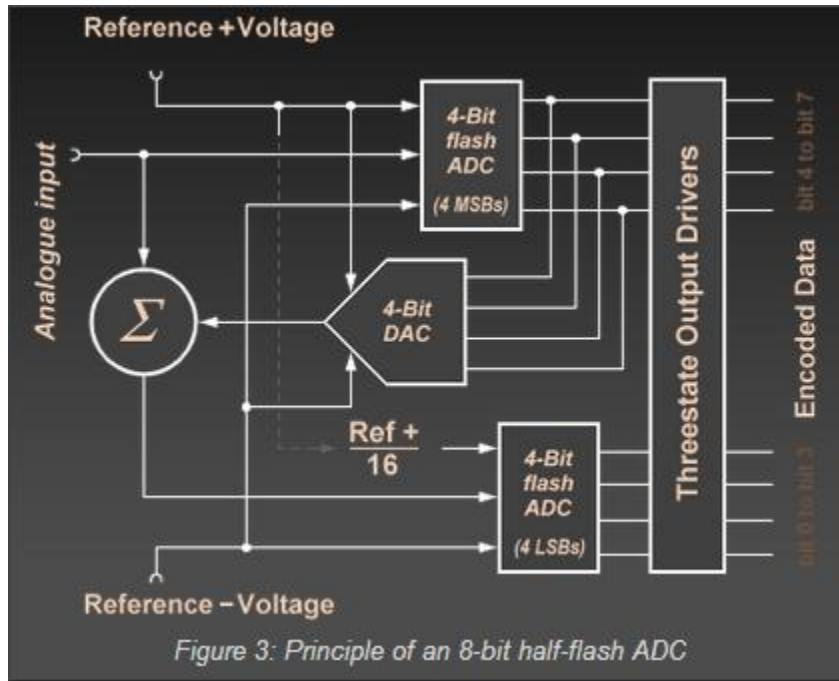


Figure 3: Principle of an 8-bit half-flash ADC

By performing the conversion in two steps it is possible to reduce the complexity of flash converters, at the expense of some loss of speed. This half-flash converter uses 30 comparators to achieve an 8-bit precision, compared with 25530 comparators for a full 8-Bit flash ADC.

Tracking ADC

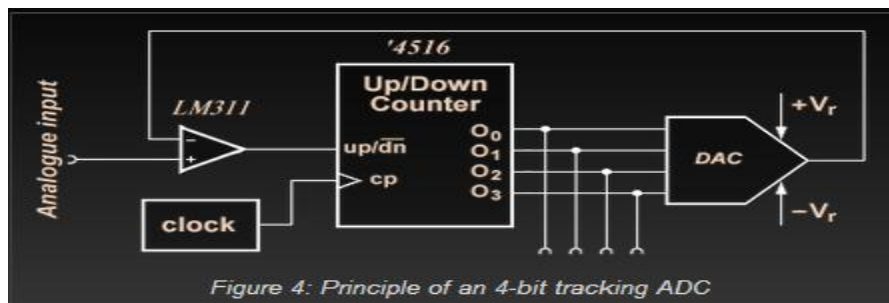


Figure 4: Principle of a 4-bit tracking ADC

The tracking ADC is one of a number of techniques which employ a DAC in a negative feedback loop. When the DAC output is below the analogue input the up/dn input is high and the counter counts up. When the DAC output is over the analogue input the up/dn input is low and the counter counts down alternatively.

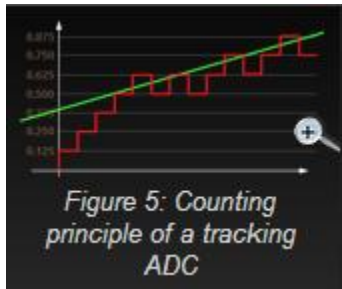


Figure 5: Counting principle of a tracking ADC

The tracking ADC is convenient for slow changes of the analogue input only. Up to $2n$ clock periods required before digital output is valid following a large change in analogue input.

Successive Approximation (SAR- ADC)

Although there are many variations in the implementation of a SAR ADC, the basic architecture is quite simple. To implement the binary search algorithm, the n -bit register is first set to midscale (that is, $100\dots 00$, where the MSB is set to '1'). This forces the DAC output (V_{DAC}) to be $V_r / 2$, where V_r is the reference voltage provided to the ADC.

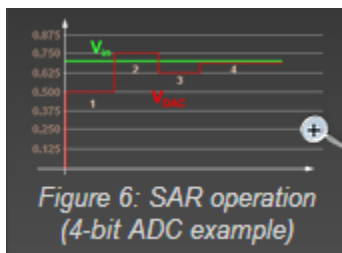


Figure 6: SAR operation (4-bit ADC example)

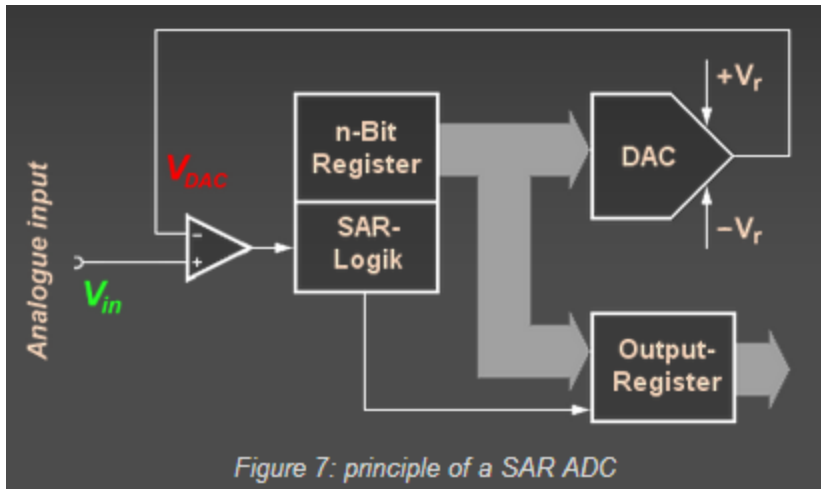


Figure 7: principle of a SAR ADC

Figure 7: principle of a SAR ADC

A comparison is then performed to determine if V_{in} is less than or greater than V_{DAC} . If V_{in} is greater than V_{DAC} , the comparator output is a logic high or '1' and the MSB of the n-bit register remains at '1'. Conversely, if V_{in} is less than V_{DAC} , the comparator output is a logic low and the MSB of the register is cleared to logic '0'. The SAR control logic then moves to the next bit down, forces that bit high, and does another comparison. The sequence continues all the way down to the LSB. Once this is done, the conversion is complete, and the n-bit digital word is available in the output register.

Source: <http://www.radartutorial.eu/17.bauteile/bt45.en.html>