

BAND PASS FILTERS


Band Pass Filter

A band-pass filter is a circuit which is designed to pass signals only in a certain band of frequencies while attenuating all signals outside this band. The parameters of importance in a bandpass filter are the high and low cut-off frequencies (f_H and f_L), the bandwidth (BW), the centre frequency f_c , centre-frequency gain, and the selectivity or Q .

There are basically two types of bandpass filters viz wide bandpass and narrow bandpass filters. Unfortunately, there is no set dividing line between the two. However, a bandpass filter is defined as a wide bandpass if its figure of merit or quality factor Q is less than 10 while the bandpass filters with $Q > 10$ are called the narrow bandpass filters. Thus Q is a measure of selectivity, meaning the higher the value of Q the more selective is the filter, or the narrower is the bandwidth (BW). The relationship between Q , 3-dB bandwidth, and the centre frequency f_c is given by an equation

For a wide bandpass filter the centre frequency can be defined as where f_H and f_L are respectively the high and low cut-off frequencies in Hz. In a narrow bandpass filter, the output voltage peaks at the centre frequency f_c .


Wide Bandpass Filter

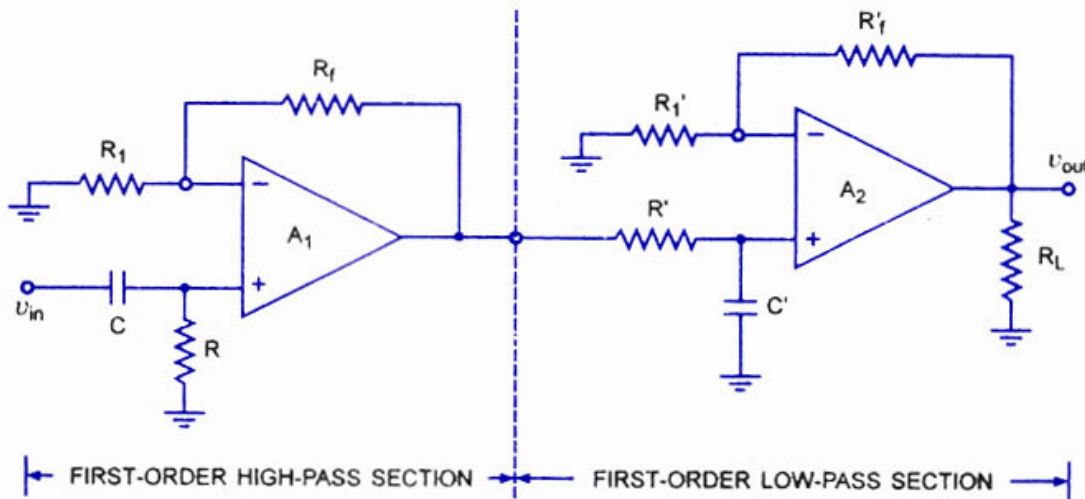

Circuit Diagram

Wide Band Pass Filter

A wide bandpass filter can be formed by simply cascading high-pass and low-pass sections and is generally the choice for simplicity of design and performance though such a circuit can be realized by a number of possible circuits. To form a ± 20 db/decade bandpass filter, a first-order high-pass and a first-order low-pass sections are cascaded; for a ± 40 db/decade bandpass filter, second-order high-pass filter and a second-order low-pass filter are connected in series, and so on. It means that, the order of the bandpass filter is governed by the order of the high-pass and low-pass filters it consists of.

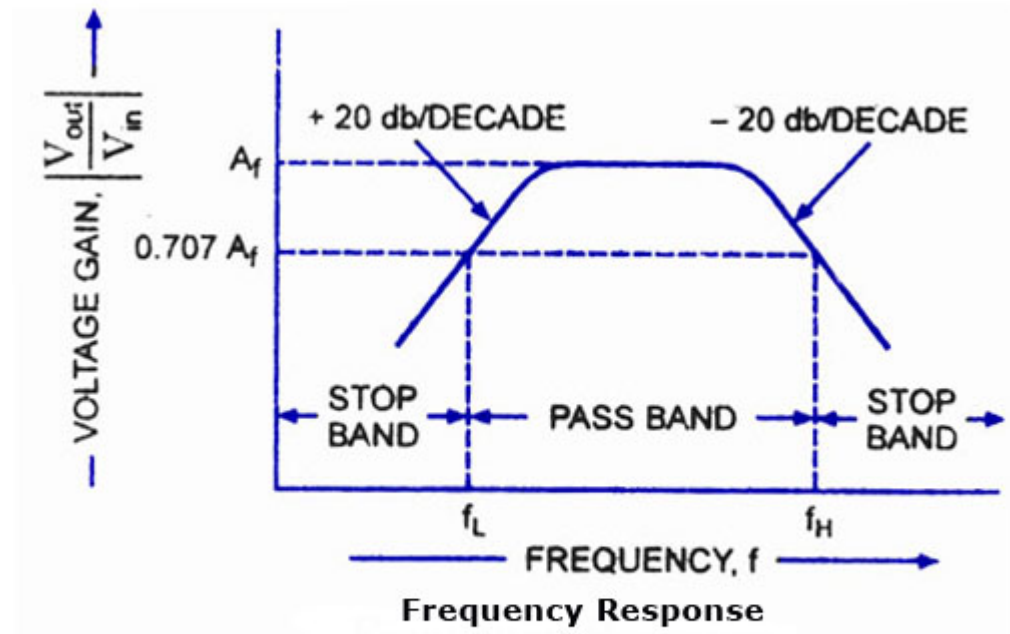


Frequency Response wide bandpass filter


www.CircuitsToday.com

A ± 20 db/decade wide bandpass filter composed of a first-order high-pass filter and a first-order low-pass filter, is illustrated in fig. (a). Its frequency response is illustrated in fig. (b).

Narrow Bandpass Filter.

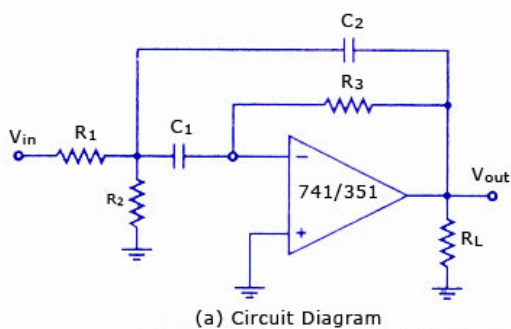

(a) Circuit Diagram

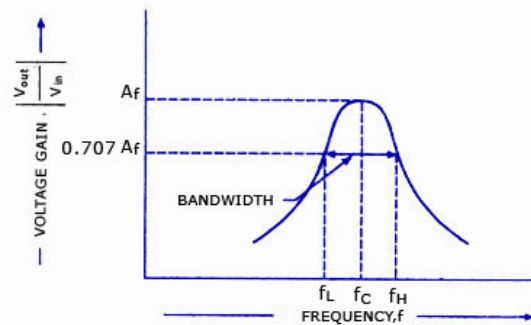

(b) Frequency Response

Multiple Feedback Narrow Band-Pass Filter

Narrow Bandpass Filter

www.CircuitsToday.com

A narrow bandpass filter employing multiple feedback is depicted in figure. This filter employs only one op-amp, as shown in the figure. In comparison to all the filters discussed so far, this filter has some unique features that are given below.

- 1. It has two feedback paths, and this is the reason that it is called a multiple-feedback filter.**
- 2. The op-amp is used in the inverting mode.**

The frequency response of a narrow bandpass filter is shown in fig(b).

Generally, the narrow bandpass filter is designed for specific values of centre frequency f_c and Q or f_c and BW. The circuit components are determined from the following relationships. For simplification of design calculations each of C_1 and C_2 may be taken equal to C .

$$R_1 = Q/2 \pi f_c C A_f$$

$$R_2 = Q/2 \pi f_c C (2Q^2 - A_f)$$

$$\text{and } R_3 = Q / \pi f_c C$$

where A_f , is the gain at centre frequency and is given as

$$A_f = R_3 / 2R_1$$

The gain A_f however must satisfy the condition $A_f < 2 Q^2$.

The centre frequency f_c of the multiple feedback filter can be changed to a new frequency f'_c without changing, the gain or bandwidth. This is achieved simply by changing R_2 to R'_2 so that

$$R'_2 = R_2 [f_c/f'_c]^2$$

Source : <http://www.circuitstoday.com/band-pass-filters>