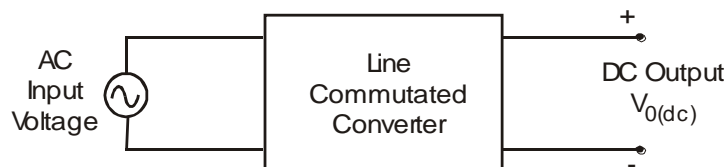


# CONTROLLED RECTIFIERS

## 4.1 Line Commutated AC to DC converters



- Type of input: Fixed voltage, fixed frequency ac power supply.
- Type of output: Variable dc output voltage
- Type of commutation: Natural / AC line commutation

### 4.1.1 Different types of Line Commutated Converters

- AC to DC Converters (Phase controlled rectifiers)
- AC to AC converters (AC voltage controllers)
- AC to AC converters (Cyclo converters) at low output frequency

### 4.1.2 Differences Between Diode Rectifiers & Phase Controlled Rectifiers

- The diode rectifiers are referred to as uncontrolled rectifiers .
- The diode rectifiers give a fixed dc output voltage .
- Each diode conducts for one half cycle.
- Diode conduction angle =  $180^0$  or  $\pi$  radians.
- We cannot control the dc output voltage or the average dc load current in a diode rectifier circuit

Single phase half wave diode rectifier gives an

$$\text{Average dc output voltage } V_{o\ dc} = \frac{V_m}{\pi}$$

Single phase full wave diode rectifier gives an

$$\text{Average dc output voltage } V_{o\ dc} = \frac{2V_m}{\pi}$$

## 4.2 Applications of Phase Controlled Rectifiers

- DC motor control in steel mills, paper and textile mills employing dc motor drives.
- AC fed traction system using dc traction motor.
- Electro-chemical and electro-metallurgical processes.
- Magnet power supplies.
- Portable hand tool drives

### 4.3 Classification of Phase Controlled Rectifiers

- Single Phase Controlled Rectifiers.
- Three Phase Controlled Rectifiers

#### 4.3.1 Different types of Single Phase Controlled Rectifiers.



- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
- Using a center tapped transformer.
- Full wave bridge circuit.
- Semi converter.
- Full converter.

#### 4.3.2 Different Types of Three Phase Controlled Rectifiers

- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
- Semi converter (half controlled bridge converter).
- Full converter (fully controlled bridge converter).
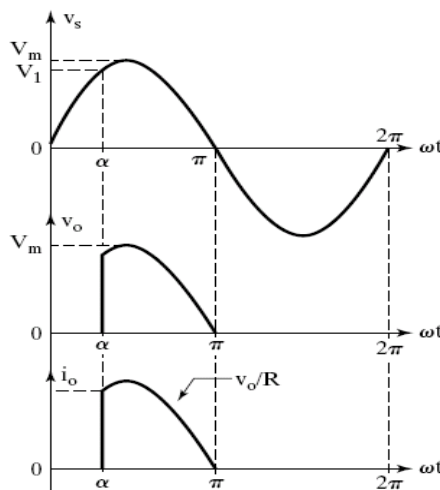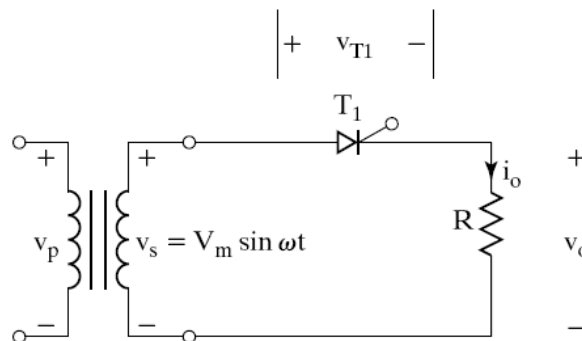
### 4.4 Principle of Phase Controlled Rectifier Operation

Single Phase Half-Wave Thyristor Converter with a Resistive Load



## Equations:

$$v_s = V_m \sin \omega t = \text{i/p ac supply voltage}$$

$$V_m = \text{max. value of i/p ac supply voltage}$$

$$V_s = \frac{V_m}{\sqrt{2}} = \text{RMS value of i/p ac supply voltage}$$

$$v_o = v_L = \text{output voltage across the load}$$

When the thyristor is triggered at  $\omega t = \alpha$

$$v_o = v_L = V_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

$$i_o = i_L = \frac{v_o}{R} = \text{Load current; } \omega t = \alpha \text{ to } \pi$$

$$i_o = i_L = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

$$\text{Where } I_m = \frac{V_m}{R} = \text{max. value of load current}$$

### 4.4.1 To Derive an Expression for the Average (DC) Output Voltage across the Load

$$V_{O\ dc} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d \omega t ;$$

$$v_o = V_m \sin \omega t \text{ for } \omega t = \alpha \text{ to } \pi$$

$$V_{O\ dc} = V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d \omega t$$

$$V_{O\ dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d \omega t$$

$$V_{O\ dc} = \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d \omega t$$

$$V_{O\ dc} = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\pi} \right]$$

$$V_{O\ dc} = \frac{V_m}{2\pi} -\cos \pi + \cos \alpha ; \cos \pi = -1$$

$$V_{O\ dc} = \frac{V_m}{2\pi} 1 + \cos \alpha ; V_m = \sqrt{2} V_s$$

Maximum average (dc) o/p  
voltage is obtained when  $\alpha = 0$   
and the maximum dc output voltage

$$V_{dc \text{ max}} = V_{dm} = \frac{V_m}{2\pi} (1 + \cos 0) ; \cos 0 = 1$$

$$\therefore V_{dc \text{ max}} = V_{dm} = \frac{V_m}{\pi}$$

$$V_{O \text{ dc}} = \frac{V_m}{2\pi} (1 + \cos \alpha) ; V_m = \sqrt{2}V_s$$

The average dc output voltage can be varied  
by varying the trigger angle  $\alpha$  from 0 to a  
maximum of  $180^\circ$   $\pi$  radians

We can plot the control characteristic

$V_{O \text{ dc}}$  vs  $\alpha$  by using the equation for  $V_{O \text{ dc}}$