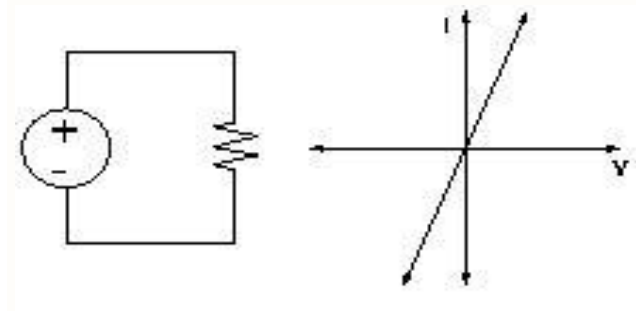


## Diodes

### **The Basic Diode Theory :**

Diodes can be defined as non-linear devices. That is we can not apply superposition to circuits containing diodes. By Ohms law, when a voltage is applied across a resistor, the current flows inproportion to the voltage and the proportionality factor is constant. The voltage- current (VI) characteristic for a resistor is shown in Figure 1and is expressed analytically by **V =**

$$\mathbf{I \cdot R, I=V/R}$$



**Figure 1: Resistor circuit and its V-I characteristics**


The V-I characteristics of a diode is shown in figure 2 and is described analytically by the equation .

$$I = I_s \left( e^{\frac{qV_D}{KTq}} - 1 \right)$$

Where  $I_s$  is the reverse saturation current, a small ( $\approx 10^{-9}$  A ) current will occur at the negativevoltage region.  $q / KT$  is a constant depends on temperature  $\approx 1/0.026V$  at room temperature. **VD** is the voltage occurred across the diode and


$\eta$

is the dimensionless constant determined by the type of the diode (Silicon, Germanium, etc.)

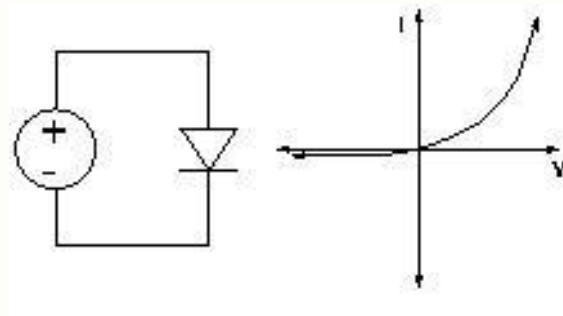

**Figure 2: Diode circuit and its V-I characteristics**

For the non-linearity of a diode, consider the circuit shown in Figure 3

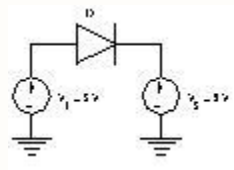

**Figure 3: A diode circuit with 2 voltage sources.**

When **V1** and **V2** are applied simultaneously, the voltage across D is -3 V and the resulting current is very close to  $-I_s$ . If superposition is applied, we get

**V1** produces 2 V across D and  $I_1 = 2190 I_s$  **V2** Produces -5 V across D and  $I_2 = -I_s$ .

If we add these two currents, we will get  $I = 2189 I_s$ . which is an incorrect

current. Since the superposition principle does not apply, we can say that a diode is a non-linear element.

Source:

<http://www.electronicsandcommunications.com/2013/03/diodes-lecture-notes.html>