

## FUNCTION GENERATOR IC 8038


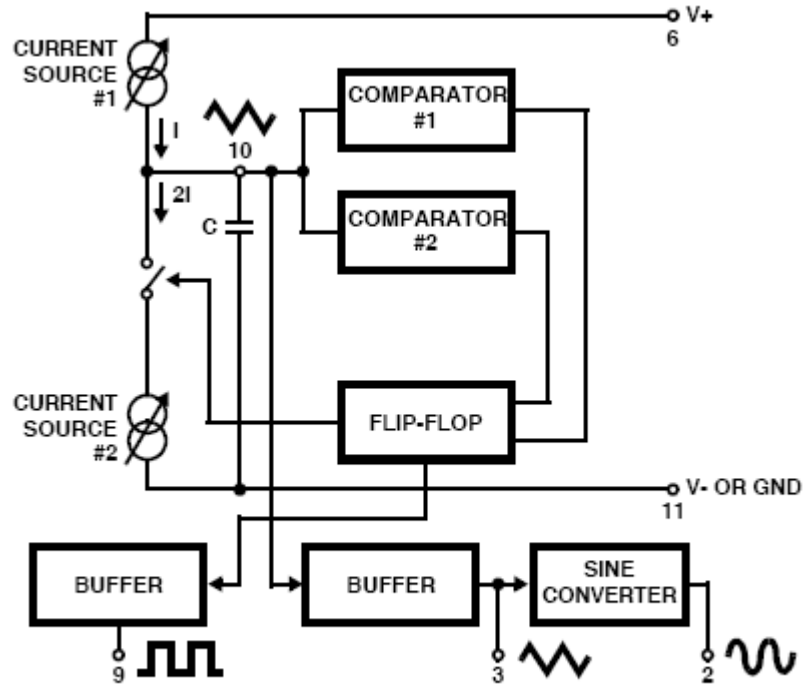


Fig: Functional block diagram of Function generator

### Output Waveform:

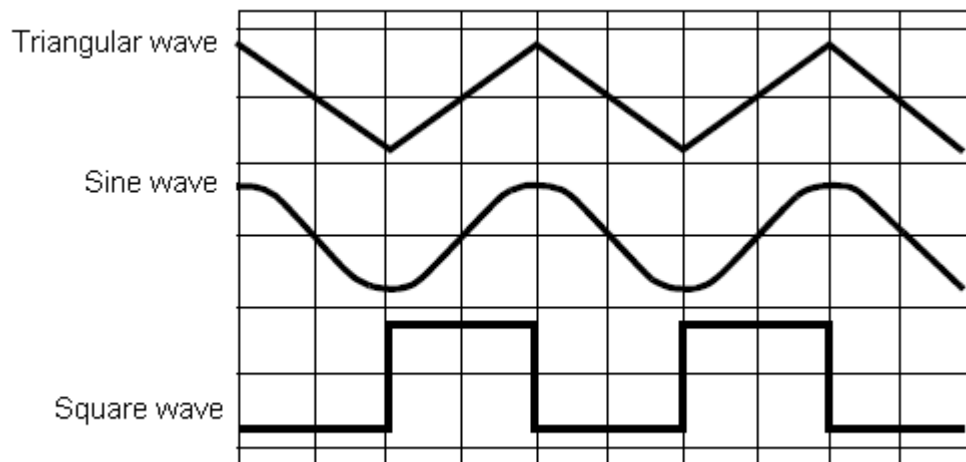

It consists of two current sources, two comparators, two buffers, one FF and a sine wave converter.

Pin description:

Pin 1 & Pin 12: Sine wave adjusts:

The distortion in the sine wave output can be reduced by adjusting the 100K $\Omega$  pots connected between pin12 & pin11 and between pin 1 & 6.

Pin 2 Sine Wave Output:

Sine wave output is available at this pin. The amplitude of this sine wave is 0.22 V<sub>cc</sub>.

Where  $\pm 5V \leq V_{cc} \leq \pm 15 V$ .

Pin 3 Triangular Wave output:

Triangular wave is available at this pin. The amplitude of the triangular wave is 0.33V<sub>cc</sub>.

Where  $\pm 5V \leq V_{cc} \leq \pm 15 V$ .

Pin 4 & Pin 5 Duty cycle / Frequency adjust:

The symmetry of all the output wave forms & 50% duty cycle for the square wave output is adjusted by the external resistors connected from V<sub>cc</sub> to pin 4. These external resistors & capacitors at pin 10 will decide the frequency of the output wave forms.

Pin 6 + V<sub>cc</sub>:

Positive supply voltage the value of which is between 10 & 30V is applied to this pin.

Pin 7 : FM Bias:

This pin along with pin no8 is used to TEST the IC 8038.

Pin9 : Square Wave Output:

A square wave output is available at this pin. It is an open collector output so that this pin can be connected through the load to different power supply voltages. This arrangement is very useful in making the square wave output.

Pin 10 : Timing Capacitors:

The external capacitor C connected to this pin will decide the output frequency along with the resistors connected to pin 4 & 5.

Pin 11 :  $-V_{EE}$  or Ground:

If a single polarity supply is to be used then this pin is connected to supply ground & if ( $\pm$ ) supply voltages are to be used then (-) supply is connected to this pin.

Pin 13 & Pin 14: NC (No Connection)

Important features of IC 8038:

1. All the outputs are simultaneously available.
2. Frequency range : 0.001Hz to 500kHz
3. Low distortion in the output wave forms.
4. Low frequency drift due to change in temperature.
5. Easy to use.

Parameters:

(i) Frequency of the output wave form:

- The output frequency dependent on the values of resistors R1 & R2 along with the external capacitor C connected at pin 10.
- If  $R_A = R_B = R$  & if  $R_C$  is adjusted for 50% duty cycle then

$$f_o = \frac{0.3}{RC} ; \quad R_A = R_1, R_B = R_3, R_C = R_2$$

(ii) Duty cycle / Frequency Adjust : (Pin 4 & 5):

Duty cycle as well as the frequency of the output wave form can be adjusted by controlling the values of external resistors at pin 4 & 5.

- The values of resistors  $R_A$  &  $R_B$  connected between  $V_{cc}$  \* pin 4 & 5 respectively along with the capacitor connected at pin 10 decide the frequency of the wave form.
- The values of  $R_A$  &  $R_B$  should be in the range of  $1k\Omega$  to  $1M\Omega$ .

(iii) FM Bias:

- The FM Bias input (pin7) corresponds to the junction of resistors  $R_1$  &  $R_2$ .
- The voltage  $V_{in}$  is the voltage between  $V_{cc}$  & pin8 and it decides the output frequency.
- The output frequency is proportional to  $V_{in}$  as given by the following expression  
For  $R_A = R_B$  (50% duty cycle).

$$f_o = \frac{1.5V_{in}}{CRAV_{cc}} \quad ; \text{ where } C \text{ is the timing capacitor}$$

- With pin 7 & 8 connected to each other the output frequency is given by

$$f_o = \frac{0.3}{RC}$$

where  $R = R_A = R_B$  for 50% duty cycle.

- This is because  $V_{in} = \frac{R_1}{R_1 + R_2} V_{cc}$

(iv) FM Sweep input (pin 8):

- This input should be connected to pin 7, if we want a constant output frequency.
- But if the output frequency is supposed to vary, then a variable dc voltage should be applied to this pin.
- The voltage between  $V_{cc}$  & pin 8 is called  $V_{in}$  and it decides the output frequency as,

$$f_o = \frac{1.5 V_{in}}{C R_A V_{cc}}$$

A potentiometer can be connected to this pin to obtain the required variable voltage required to change the output frequency.

Source : <https://aihteienotes.files.wordpress.com/2014/07/lic-notes.doc>