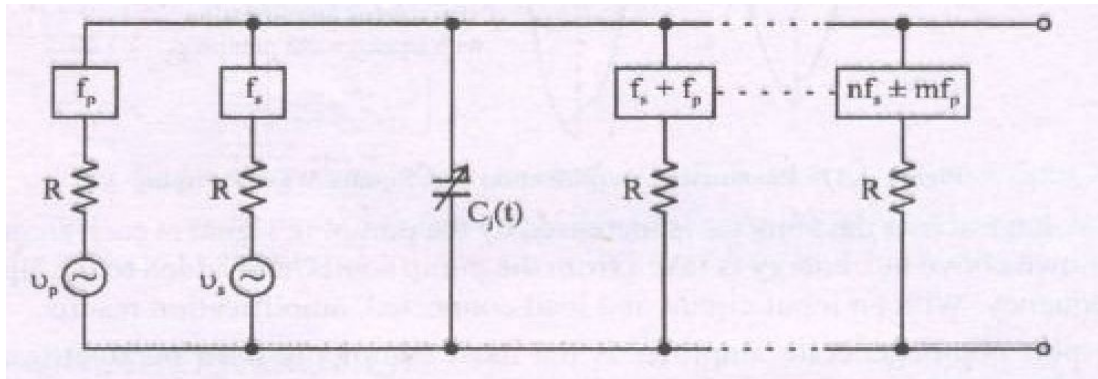


MANLEY – ROWE RELATIONS:

For the determination of maximum gain of the parametric amplifier, a set of power conservation relations known as "Manley-Rowe" relations are quite useful.



two sinusoidal signals f_p and f_s applied across a lossless time varying non-linear capacitance $C_j(t)$. At the output of this varying capacitance, harmonics of the two frequencies f_p and f_s are generated.

These harmonics are separated using band-pass filters having very narrow bandwidth.


The power at these harmonic frequencies is dissipated in the respective resistive loads.

From the law of conservation of energy, we have

$$\sum_{m=-\infty}^{\infty} \sum_{n=0}^{\infty} \frac{n P_{mn}}{nf_s + mf_p} = 0$$

$$\sum_{m=0}^{\infty} \sum_{n=-\infty}^{\infty} \frac{m P_{mn}}{nf_s + mf_p} = 0$$

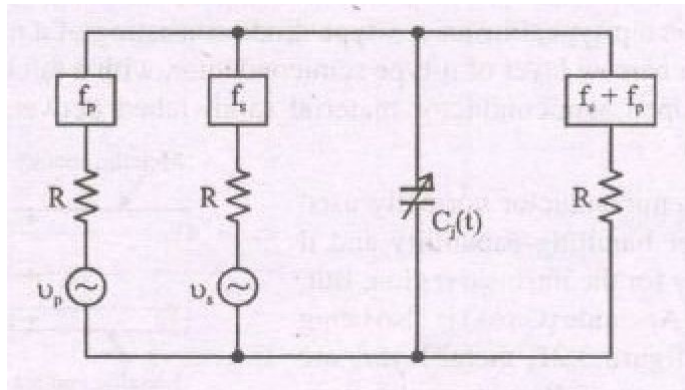The above relations are called "Manley-Rowe" power conservation equations. When The power is supplied by the two generators, then P_{mn} is positive. In this case, power will flow into the non-linear capacitance. If it is the other way, then P_{mn} is negative.



As an example, let us consider the case when the power output flow is allowed at the sum frequency $f_p + f_s$ only, with all the remaining harmonics being open circuited. With the above rest ructions, the quantities 'm' and 'n' can take on values -1,0 and respectively.

$$\frac{P_{01}}{f_s} + \frac{P_{11}}{f_s + f_p} = 0$$

and

$$\frac{P_{10}}{f_p} + \frac{P_{11}}{f_s + f_p} = 0$$

The powers P_{01} and P_{10} are considered positive, whereas P_{11} is considered negative. \therefore The power gain defined as the power output from the non-linear capacitor delivered to the load at sum frequency to that power received by it at a frequency f_s is given by

$$G_p = \frac{P_{11}}{P_{01}} = \frac{f_s + f_p}{f_s} \text{ (for modulator)}$$

Thus the power gain is the ratio of output to input frequency. This type of parametric device is called "Sum-frequency parametric amplifier" or "up-converter".

On the other hand, if the signal frequency is $f_p + f_s$ and output frequency is f_s then

$$G_p = \frac{f_s}{f_p + f_s} \text{ (for demodulator)}$$

This type of parametric device will now be called "parametric down-converter" and the power gain becomes power attenuation.

Source : <http://elearningatria.files.wordpress.com/2013/10/ece-v-microwaves-and-radar-10ec54-notes.pdf>