

# MEASURING L: SINUSOIDAL RESPONSE AND RLC RESONANCE

## 1. Exercise

Consider the series RL circuit of Figure 5 driven by a sinusoidal voltage.

Using your favorite method, derive an expression for the ratio  $S = \left| \frac{V_{out}}{V_{in}} \right|$  of the magnitude of the voltage across the capacitor/inductor to the magnitude of the voltage across the voltage source as a function of frequency. To model a real inductor, include an internal resistance  $R_L$  in series with the inductor, and include this resistor in the voltage drop across the inductor. Use your expression for  $S$  to find an expression for the inductance  $L$  in terms of  $S$ ,  $R$ ,  $R_L$ , and  $\omega$ . It should be noted that there is nothing about this general approach that is specific to inductors. It works just as well for measuring capacitance.

## 2. Simulation

Use a small signal AC analysis to generate a plot of  $S$  vs. frequency for the RL circuit you analyzed in the Exercise above. Include the internal resistance of the inductor. If you use a source amplitude of 1 V, then values

of the voltage across the inductor and its internal resistance (with units removed) are also values of  $S$ . Set up the simulation, guessing values for  $L$  and  $R_L$ . You will refine it as you work through the following experiment.

### 3. Experiment

First, measure the internal resistance  $R_L$  of the inductor. Give an uncertainty with your result. (Presumably, you know the resistance  $R$  of the resistor you are using. If not, measure that, too.) Then, use the function generator to drive your series RL circuit with a sinusoidal wave form. Use one channel of the oscilloscope to measure  $V_{in}$  and the other to measure  $V_{out}$ .


Compare  $V_{in}$  and  $V_{out}$  at various frequencies. How well do your measurements compare with your theoretical calculation and spice simulation? Remember that  $\omega = 2\pi f$ . Use a measurement of  $S$  in your theoretical calculation to find  $L$ . Report an uncertainty with your result. Be sure to measure your  $S$  value at good frequency. What does "good" mean here?<sup>2</sup> How far off were you in your measurement of  $L$  of Section 1? Can this discrepancy be attributed to ignoring the internal resistance of the inductor? Explain.

# RLC Resonance

## 1. Exercise

At resonance, the capacitive and inductive reactances cancel, the phase angle  $\phi$  is 0, and the voltage across the resistor is maximal (as are the current and  $S$ ). Derive an expression for the resonant frequency  $f_o$  of a series RLC circuit in terms of  $L$  and  $C$ .

## 2. Simulation

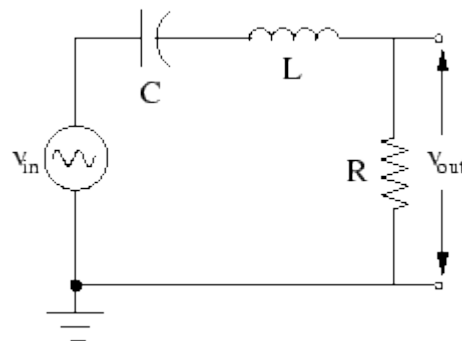

**Figure 6:** Series RLC circuit.

3. Set up an AC analysis of the circuit shown in Figure 6. Produce plots of  $S$  and  $\phi$  as a function of frequency, and note the predicted resonant frequency. Investigate and report on the dependence of the plots and the resonant frequency on the resistance  $R$ , and explain.

#### 4. Experiment

Set up the circuit shown in Figure 6. Measure the voltage across the source  $V_{in}$  with one channel the oscilloscope and  $V_{out}$  with the other. Dial up X-Y mode on the time base knob to plot  $V_{in}$  vs.  $V_{out}$ . At resonance, these two signals are in phase. In X-Y mode, this looks like a straight line. At any other frequency, the oscilloscope trace resembles an ellipse.

In time base mode, you can look for the frequency at which the voltage across the resistor  $V_{out}$  is maximal. Report an uncertainty in your result. Compare your result with your theoretical prediction using your best measured values of  $C$  and  $L$ .

Source: <http://webpages.ursinus.edu/lriley/ref/circuits/node3.html>