

## MONOLITHIC PLL IC 565 APPLICATIONS

The output from a PLL system can be obtained either as the voltage signal  $v_c(t)$  corresponding to the error voltage in the feedback loop, or as a frequency signal at VCO output terminal. The voltage output is used in frequency discriminator applications whereas the frequency output is used in signal conditioning, frequency synthesis or clock recovery applications.


Consider the case of voltage output. When PLL is locked to an input frequency, the error voltage  $v_c(t)$  is proportional to  $(f_s - f_o)$ . If the input frequency is varied as in the case of FM signal,  $v_c$  will also vary in order to maintain the lock. Thus the voltage output serves as a frequency discriminator which converts the input frequency changes to voltage changes.

In the case of frequency output, if the input signal is comprised of many frequency components corrupted with noise and other disturbances, the PLL can be made to lock, selectively on one particular frequency component at the input. The output of VCO would then regenerate that particular frequency (because of LPF which gives output for beat frequency) and attenuate heavily other frequencies. VCO output thus can be used for regenerating or reconditioning a desired frequency signal (which is weak and buried in noise) out of many undesirable frequency signals.


Some of the typical applications of PLL are discussed below.
 
### (i) Frequency Multiplier:

- Frequency divider is inserted between the VCO & phase comparator. Since the output of the divider is locked to the  $f_{IN}$ , VCO is actually running at a multiple of the input frequency.
- The desired amount of multiplication can be obtained by selecting a proper divide-by-N network, where N is an integer.



(a) Block Diagram

 


(b) Connection Diagram For Multiple Frequency Multiplier

 (ii) Frequency Shift Keying (FSK) demodulator:

In computer peripheral & radio (wireless) communication the binary data or code is transmitted by means of a carrier frequency that is shifted between two preset frequencies. Since a carrier frequency is shifted between two preset frequencies, the data transmission is said to use a FSK. The frequency corresponding to logic 1 & logic 0 states are commonly called the mark & space frequency.

For example, When transmitting teletype writer information using a modulator-demodulator (modem) a 1070-1270 (mark-space) pair represents the originate signal, while a 2025-2225 Hz (mark-space) pair represents the answer signal.



FSK Generator:

- The FSK generator is formed by using a 555 as an astable multivibrator, whose frequency is controlled by the state of transistor Q1.
- In other words, the output frequency of the FSK generator depends on the logic state of the digital data input.
- 150 Hz is one of the standard frequencies at which the data are commonly transmitted.
- When the input is logic 1, the transistor Q1 is off. Under the condition, 555 timer works in its normal mode as an astable multivibrator i.e., capacitor C charges through  $R_A$  &  $R_B$  to  $2/3 V_{cc}$  & discharges through  $R_B$  to  $1/3 V_{cc}$ .

Thus capacitor C charges & discharges between  $2/3 V_{cc}$  &  $1/3 V_{cc}$  as long as the input is logic 1.

- The frequency of the output waveform is given by,

$$1.45$$

$$f_o = \frac{1}{(R_A + 2R_B)C} = 1070 \text{ Hz (mark frequency)}$$

$$(R_A + 2R_B)C$$

- When the input is logic 0, (Q1 is ON saturated) which in turn connects the resistance  $R_C$  across  $R_A$ . This action reduces the charging time of capacitor C1 increases the output frequency, which is given by,

$$1.45$$

$$f_o = \frac{1}{(R_A \parallel R_C + 2R_B)C} = 1270 \text{ Hz (space frequency)}$$

$$(R_A \parallel R_C + 2R_B)C$$


- By proper selection of resistance  $R_C$ , this frequency is adjusted to equal the space frequency of 1270 Hz. The difference between the FSK signals of 1070 Hz & 1270 Hz is 200 Hz, this difference is called “frequency shift”.
- The output 150 Hz can be made by connecting a voltage comparator between the output of the ladder filter and pin 6 of PLL.
- The VCO frequency is adjusted with R1 so that at  $f_{IN} = 1070$  Hz.

#### FSK Demodulator:

- The output of 555 FSK generator is applied to the 565 FSK demodulator.
- Capacitive coupling is used at the input to remove dc line.
- At the input of 565, the loop locks to the input frequency & tracks it between the 2 frequencies.
- R1 & C1 determine the free running frequency of the VCO, 3 stage RC ladder filter is used to remove the carrier component from the output.

In digital data communication and computer peripheral, binary data is transmitted by means of a carrier frequency which is shifted between two preset frequencies. This type of data transmission is called frequency shift keying (FSK) technique. The binary data can be retrieved using FSK

 
demodulator. The figure below shows FSK demodulator using PLL for tele-typewriter signals of 1070 Hz and 1270 Hz. As the signal appears at the input, the loop locks to the input frequency and tracks it between the two frequencies with a corresponding dc shift at the output. A three stage filter removes the carrier component and the output signal is made logic compatible by a voltage comparator.



(iii)AM Demodulation:

A PLL may be used to demodulate AM signals as shown in the figure below. The PLL is locked to the carrier frequency of the incoming AM signal. The output of VCO which has the same frequency as the carrier, but unmodulated is fed to the multiplier. Since VCO output is always  $90^\circ$  before being fed to the multiplier. This makes both the signals applied to the multiplier and the difference signals, the demodulated output is obtained after filtering high frequency components by the LPF. Since the PLL responds only to the carrier frequencies which are very

 close to the VCO output, a PLL AM detector exhibits high degree of selectivity and noise immunity which is not possible with conventional peak detector type AM modulators.



(iv) FM Demodulation:

If PLL is locked to a FM signal, the VCO tracks the instantaneous frequency of the input signal. The filtered error voltage which controls the VCO and maintains lock with the input signal is the demodulated FM output. The VCO transfer characteristics determine the linearity of the demodulated output. Since, VCO used in IC PLL is highly linear, it is possible to realize highly linear FM demodulators.

(v) frequency multiplication/division:


The block diagram shown below shows a frequency multiplier/divider using PLL. A divide by N network is inserted between the VCO output and the phase comparator input. In the locked state, the VCO output frequency  $f_o$  is given by

$f_o = Nf_s$ . The multiplication factor can be obtained by selecting a proper scaling factor N of the counter.

Frequency multiplication can also be obtained by using PLL in its harmonic locking mode. If the input signal is rich in harmonics e.g. square wave, pulse train etc., then the VCO can be directly locked to the n-th harmonic of the input signal without connecting any frequency divider in between. However, as the amplitude of the higher order harmonics becomes less, effective locking may not take place for high values of n. Typically n is kept less than 10.

The circuit of the figure above can also be used for frequency division. Since the VCO output (a square wave) is rich in harmonics, it is possible to lock the m-th harmonic of the VCO output with the input signal  $f_s$ . The output  $f_o$  of VCO is now given by

$$f_o = f_s / m$$

 


(vi) PLL Frequency Synthesis:

In digital wireless communication systems (GSM, CDMA etc), PLL's are used to provide the Local Oscillator (LO) for up-conversion during transmission, and down-conversion during reception. In most cellular handsets this function has been largely integrated into a single integrated circuit to reduce the cost and size of the handset. However due to the high performance required of base station terminals, the transmission and reception circuits are built with discrete components to achieve the levels of performance required. GSM LO modules are typically built with a Frequency Synthesizer integrated circuit, and discrete resonator VCO's.

Frequency Synthesizer manufacturers include Analog Devices, National Semiconductor and Texas Instruments. VCO manufacturers include Sirenza, Z-Communications, Inc. (Z-COMM) Principle of PLL synthesizers

A phase locked loop does for frequency what the Automatic Gain Control does for voltage. It compares the frequencies of two signals and produces an error signal which is proportional to the difference between the input frequencies. The error signal is then low pass filtered and used to drive a voltage-controlled oscillator (VCO) which creates an output frequency. The output frequency is fed through a frequency divider back to the input of the system, producing a negative feedback loop. If the output frequency drifts, the error signal will increase, driving the frequency in the opposite direction so as to reduce the error. Thus the output is *locked* to the frequency at the other input. This input is called the reference and is derived from a crystal oscillator, which is very stable in frequency. The block

diagram below shows the basic elements and arrangement of a PLL based frequency synthesizer.

 

The key to the ability of a frequency synthesizer to generate multiple frequencies is the divider placed between the output and the feedback input. This is usually in the form of a digital counter, with the output signal acting as a clock signal. The counter is preset to some initial count value, and counts down at each cycle of the clock signal. When it reaches zero, the counter output changes state and the count value is reloaded. This circuit is straightforward to implement using flip-flops, and because it is digital in nature, is very easy to interface to other digital components or a microprocessor. This allows the frequency output by the synthesizer to be easily controlled by a digital system.

Example:

Suppose the reference signal is 100 kHz, and the divider can be preset to any value between 1 and 100. The error signal produced by the comparator will only be zero when the output of the divider is also 100 kHz. For this to be the case, the VCO must run at a frequency which is 100 kHz x the divider count value. Thus it will

produce an output of 100 kHz for a count of 1, 200 kHz for a count of 2, 1 MHz for a count of 10 and so on. Note that only whole multiples of the reference frequency can be obtained with the simplest integer N dividers. Fractional N dividers are readily available

Source : <https://aihteienotes.files.wordpress.com/2014/07/lic-notes.doc>