

OP-AMP COMPARATOR

A comparator finds its importance in circuits where two voltage signals are to be compared and to be distinguished on which is stronger. A comparator is also an important circuit in the design of non-sinusoidal waveform generators as relaxation oscillators.

In an op-amp with an open loop configuration with a differential or single input signal has a value greater than 0, the high gain which goes to infinity drives the output of the op-amp into saturation. Thus, an op-amp operating in open loop configuration will have an output that goes to positive saturation or negative saturation level or switch between positive and negative saturation levels and thus clips the output above these levels. This principle is used in a comparator circuit with two inputs and an output. The 2 inputs, out of which one is a reference voltage (V_{ref}) is compared with each other.

Working of 741 IC Op-amp Comparator Circuit

Non-inverting 741 IC Op-amp Comparator Circuit


A non-inverting 741 IC op-amp comparator circuit is shown in the figure below. It is called a non-inverting comparator circuit as the sinusoidal input signal V_{in} is applied to the non-inverting terminal. The fixed reference voltage V_{ref} is give to the inverting terminal (-) of the op-amp.

When the value of the input voltage V_{in} is greater than the reference voltage V_{ref} the output voltage V_o goes to positive saturation. This is because the voltage at the non-inverting input is greater than the voltage at the inverting input.


When the value of the input voltage V_{in} is lesser than the reference voltage V_{ref} , the output voltage V_o goes to negative saturation. This is because the voltage at the non-inverting input is smaller than the voltage at the inverting input. Thus, output voltage V_o changes from positive saturation point to negative saturation point whenever the difference between V_{in} and V_{ref} changes. This is shown in the waveform below. The comparator can be called a voltage level detector, as for a fixed value of V_{ref} , the voltage level of V_{in} can be detected.

The circuit diagram shows the diodes $D1$ and $D2$. These two diodes are used to protect the op-amp from damage due to increase in input voltage. These diodes are called clamp diodes as they clamp the differential input voltages to either 0.7V or -0.7V. Most op-amps do not need clamp diodes as most of them already have built in protection. Resistance $R1$ is connected in series with input voltage V_{in}

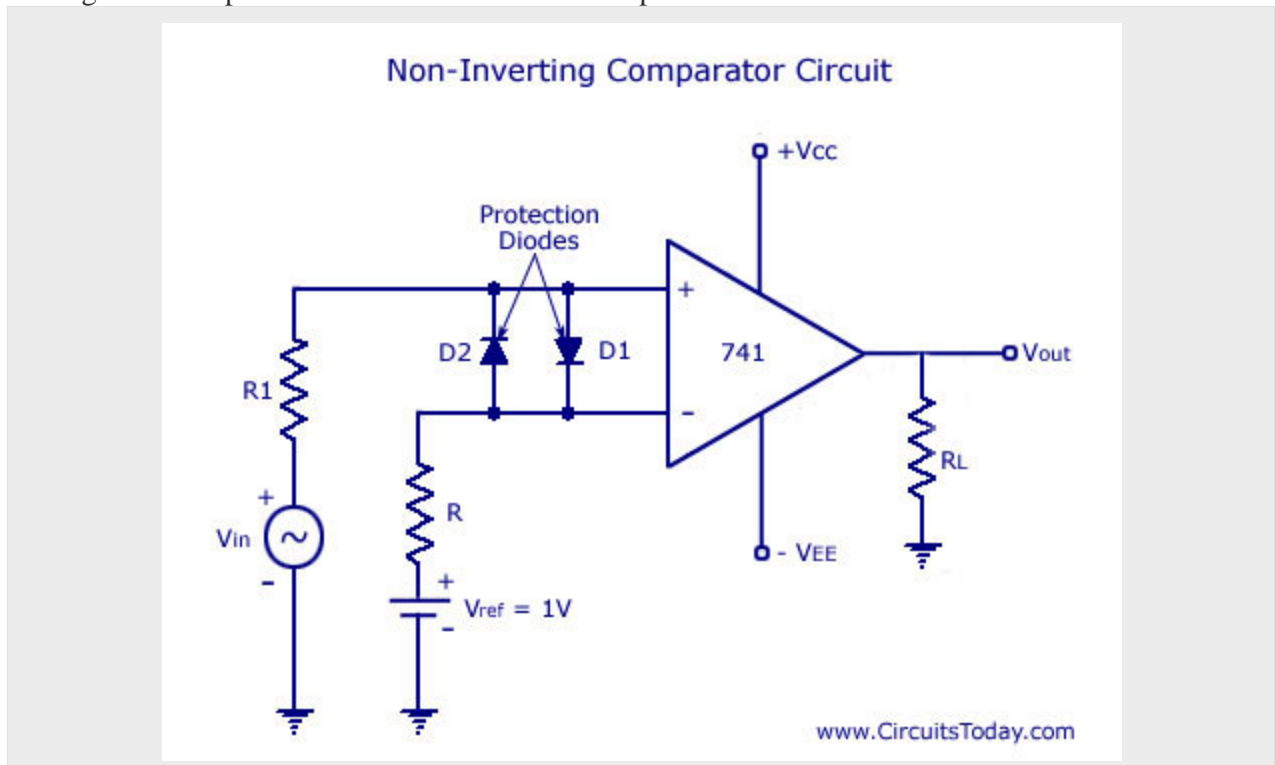and R is connected between the inverting input and reference voltage V_{ref} . R1 limits the current through the clamp diodes and R reduces the offset problem.



741 IC Non-Inverting Comparator Circuit

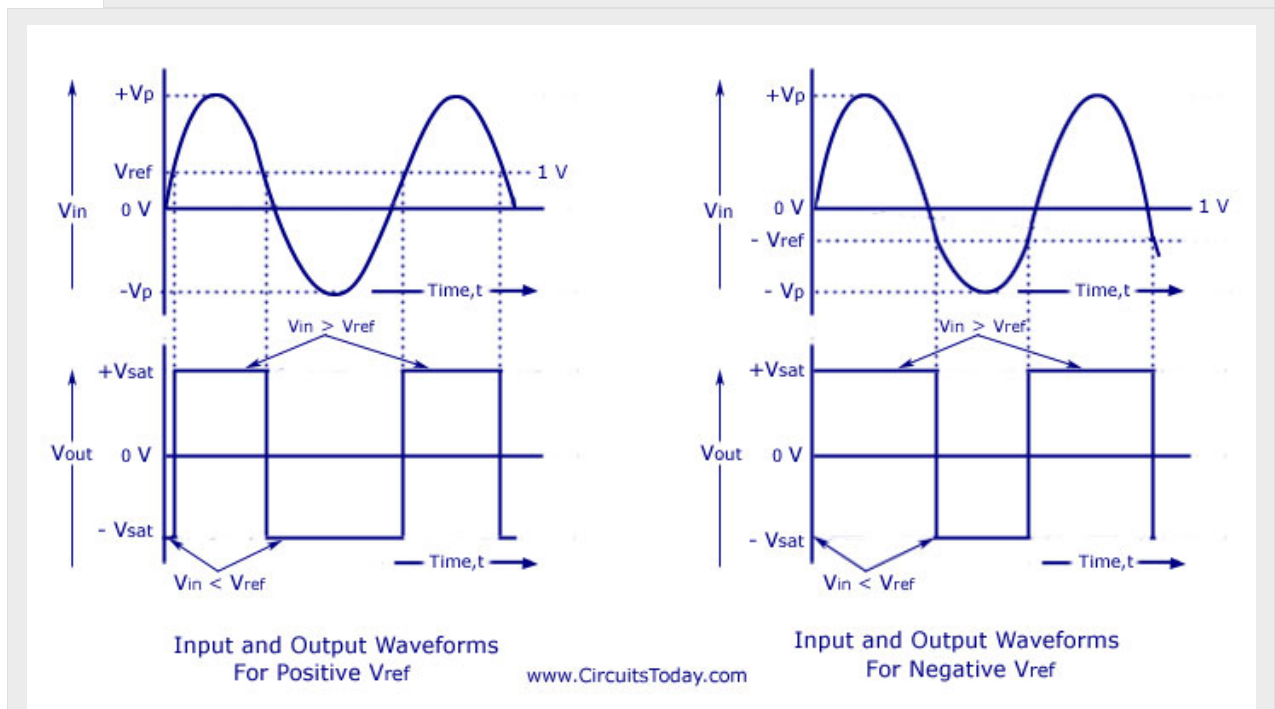

741 IC Op-Amp Non-Inverting Comparator Waveform