

RLC BAND PASS AND NOTCH FILTERS

The filters shown have their pass band and notch centered at $\omega = 1$ rad/sec, because we have chosen $R = 1 \Omega$, $C = 1$ F, and $L = 1$ H. The center of frequency is determined

by $\omega_0 = \frac{1}{\sqrt{LC}}$ for both cases. The width measured at the 3 dB points is $\Delta\omega$. The *quality factor* Q is a measure of the sharpness of the resonance and is defined as

$$Q = \frac{\omega_0}{\Delta\omega}; \quad \text{for series RLC circuits: } Q = \omega_0 L / R; \quad \text{and for parallel RLC circuits: } Q = \omega_0 RC$$

alternately we can substitute $\omega_0 = \frac{1}{\sqrt{LC}}$

With this substitution the relationship between the Q of series and parallel circuits then becomes clear.

$$\text{series: } Q = \omega_0 \frac{L}{R} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{\sqrt{L}}{R} = \frac{Z_0}{R}$$

$$\text{parallel: } Q = \omega_0 RC = \frac{1}{\sqrt{LC}} RC = \frac{R}{\sqrt{L}} = \frac{R}{Z_0}$$

$Z_0 = \sqrt{\frac{L}{C}}$ is the characteristic impedance of the LC circuit.

Units: In these calculations remember that farad \times henry = second². You will also need use the context of the equation to distinguish between ω and f , because formally they both have units of second⁻¹, so be careful!


Note also that Henry / Farad = Ohm².

Band Pass Filters


Q is also related to the dissipation (damping) in the resonant circuit.

$$Q = 2\pi \frac{(\text{energy stored})}{(\text{energy dissipated per cycle})}$$


Bode Plot of Series RLC Band-Pass Filter

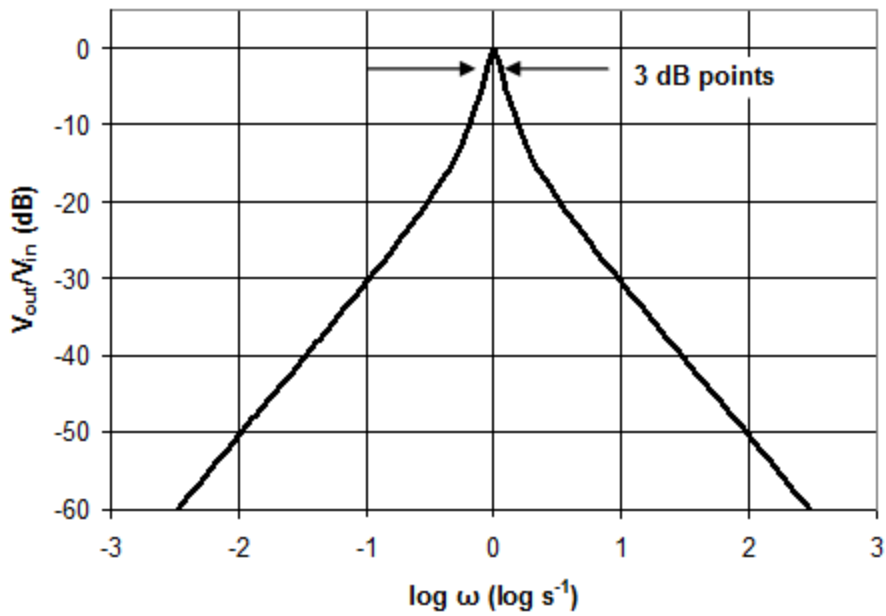

Phase of Series RLC Band-Pass Filter

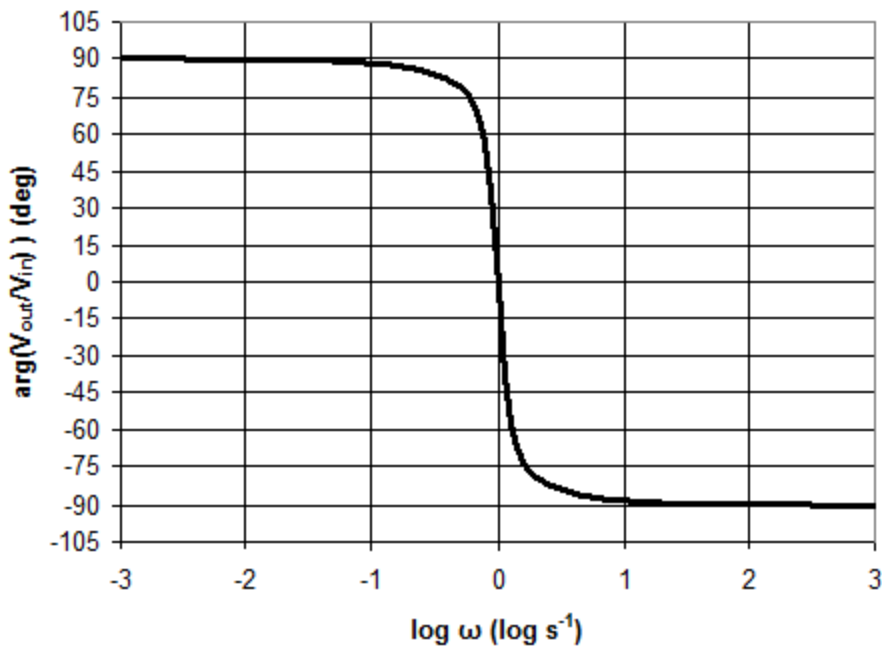

Notch Filters (Band Reject Filters)

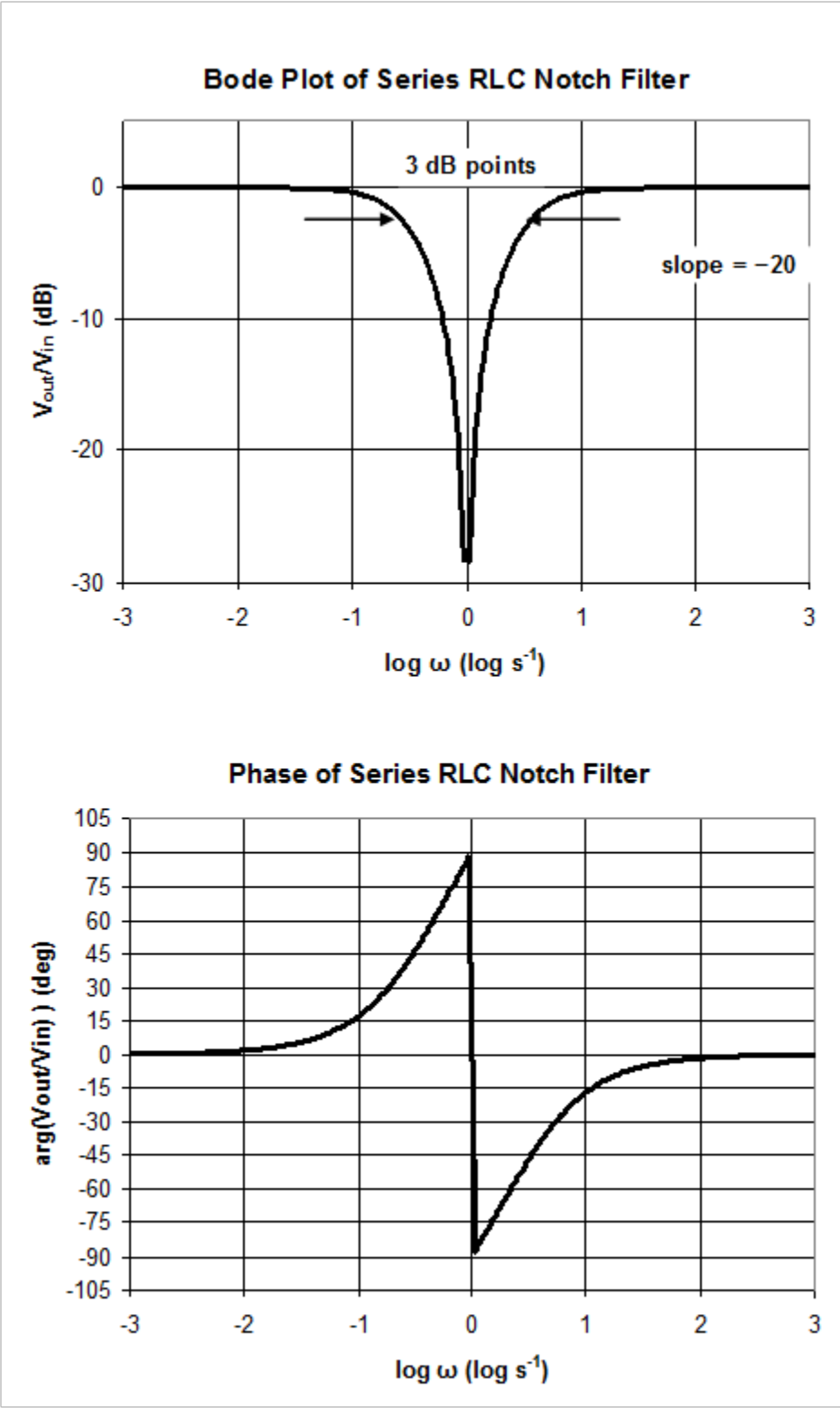

Source : http://www.nhn.ou.edu/~bumm/ELAB/Lect_Notes/AC_impedance_v2_1_1.html