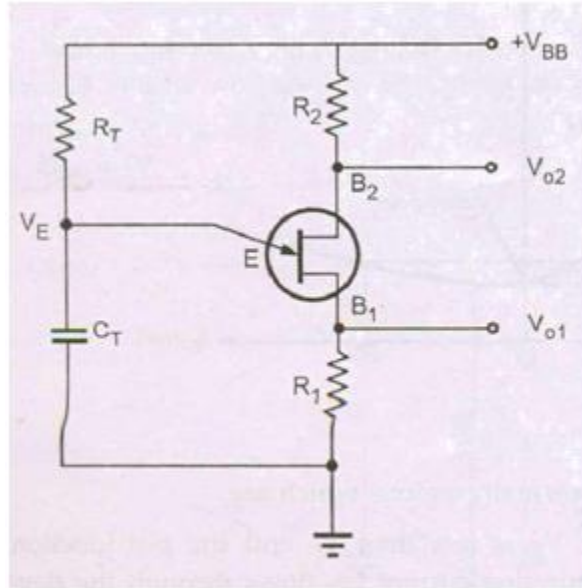


## RELAXATION OSCILLATOR




The pulse signal required to drive the digital circuits can be obtained from a single stage oscillator circuits using a particular device like unijunction transistor.

Such an oscillator which uses UJT is called UJT relaxation oscillator. The basic circuit of UJT relaxation oscillator is shown in the Fig.

The  $R_1$  and  $R_2$  are biasing resistances which are selected such that they are lower than interbase resistances  $R_{B1}$  and  $R_{B2}$ .

The resistance  $R_T$  and the capacitance  $C_T$  decide the oscillating rate. The value of  $R_T$  is so selected that the operating point of UJT remains in the negative resistance region.

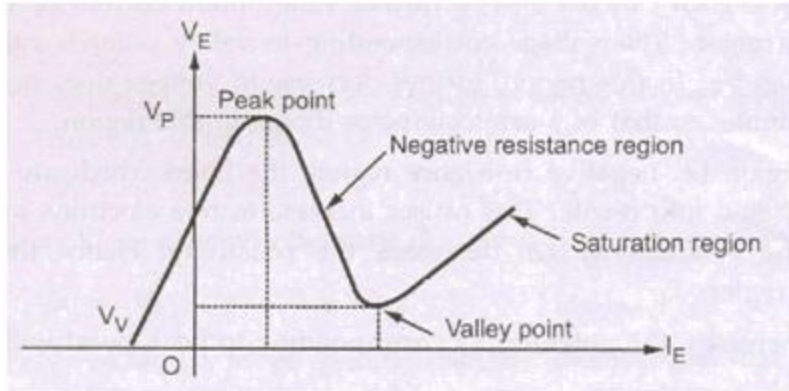The UJT characteristics and the negative resistance region of the characteristics are shown in the Fig. The characteristics of UJT show the variation between  $V$  and  $I$  where  $V_E$  is emitter voltage and  $I_E$  is emitter current.




## OPERATION

Capacitor  $C_T$  gets charged through the resistance  $R_T$  towards supply voltage  $V_{BB}$ . As long as the capacitor voltage is less than peak voltage  $V_p$  the emitter appears as an open circuit.

When the capacitor voltage  $V_c$  exceeds the voltage  $V_p$  the UJT fires. The capacitor starts discharging through  $R_1 + R_{B1}$  where  $R_{B1}$  internal base resistance. As  $R_{B1}$  is assumed negligible and hence capacitor discharges through  $R_1$ .

Due to the design of  $R_1$  this discharge is very fast, and it produces a pulse across  $R_1$ . When the capacitor voltage falls below  $V_v$  i.e.  $V_C = V_E = V_V$  the UJT gets turned OFF. The capacitor starts charging again.

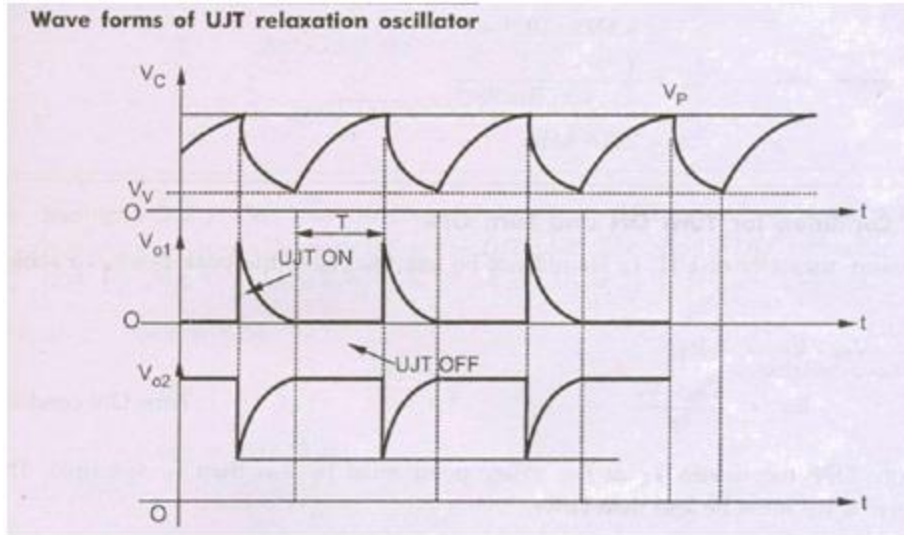The discharge time of the pulse is controlled by the time constant  $C_T R_1$  while the charging time constant by  $R_T C_T$ .



There is voltage drop across R2 and voltage rise across R1, when UJT fires. The charging equation of the capacitor is given by,

$$V_{C(t)} = V_V + V_{BB} [1 - e^{-t/R_T C_T}]$$

$$V_{C(t)} = V_P, \text{ at } t = T$$

$$V_P = V_V + V_{BB} [1 - e^{-T/R_T C_T}]$$

Source : <http://mediatoget.blogspot.in/2011/10/relaxation-oscillator.html>