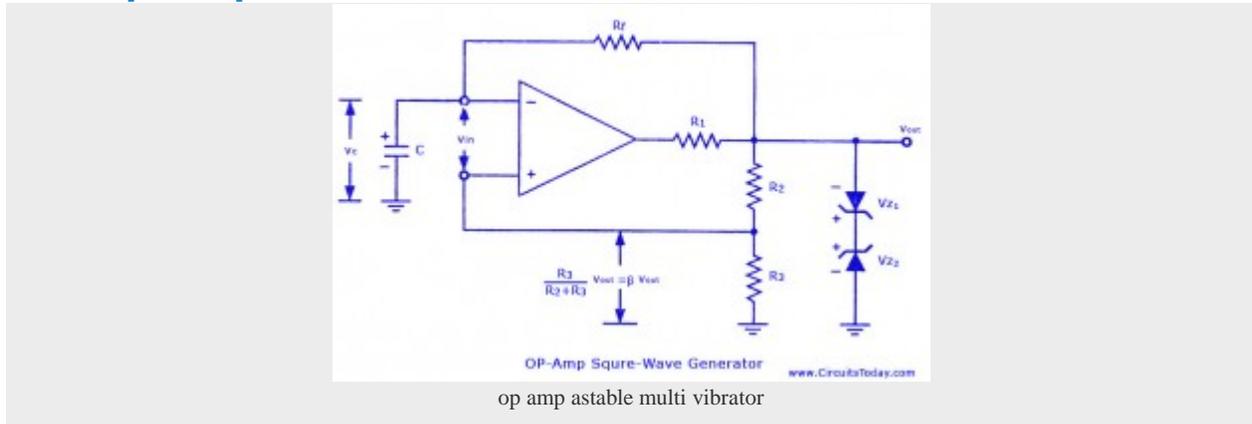


SQUARE WAVE GENERATOR USING OP-AMP

How to make an Astable or Free running Multi vibrator using 741 Op-Amp ?



The non-sinusoidal waveform generators are also called relaxation oscillators. The op-amp relaxation oscillator shown in figure is a square wave generator. In general, square waves are relatively easy to produce. Like the **UJT relaxation oscillator**, the circuit's frequency of oscillation is dependent on the charge and discharge of a capacitor C through feedback resistor R_f. The "heart" of the oscillator is an **inverting op-amp comparator**

The comparator uses positive feedback that increases the gain of the amplifier. In a comparator circuit this offers two advantages. First, the high gain causes the op-amp's output to switch very quickly from one state to another and vice-versa. Second, the use of positive feedback gives the circuit hysteresis. In the op-amp square-wave generator circuit given in figure, the output voltage v_{out} is shunted to ground by two Zener diodes Z_1 and Z_2 connected back-to-back and is limited to either V_{Z2} or $-V_{Z1}$. A fraction of the output is fed back to the non-inverting (+) input terminal. Combination of IL and C acting as a low-pass R-C circuit is used to integrate the output voltage v_{out} and the capacitor voltage v_c is applied to the inverting input terminal in place of external signal. The differential input voltage is given as $v_{in} = v_c - \beta v_{out}$

When v_{in} is positive, $v_{out} = -V_{Z1}$ and when v_{in} is negative $v_{out} = +V_{Z2}$. Consider an instant of time when $v_{in} < 0$. At this instant $v_{out} = +V_{Z2}$, and the voltage at the non-inverting (+) input terminal is βV_{Z2} , the capacitor C charges exponentially towards V_{Z2} , with a time constant $R_f C$. The output voltage remains constant at V_{Z2} until v_c equal βV_{Z2} .

When it happens, comparator output reverses to $-V_{z1}$. Now v_c changes exponentially towards $-V_{z1}$ with the same time constant and again the output makes a transition from $-V_{z1}$ to $+V_{z2}$ when v_c equals $-\beta V_{z1}$

Let $V_{z1} = V_{z2}$

The time period, T , of the output square wave is determined using the charging and discharging phenomena of the capacitor C . The voltage across the capacitor, v_c when it is charging from $-V_z$ to $+V_z$ is given by

$$V_c = [1 - (1 + \beta)]e^{-T/2\tau}$$

Where $\tau = R_f C$

The waveforms of the capacitor voltage v_c and output voltage v_{out} (or v_z) are shown in figure.


When $t = T/2$

$$V_c = +\beta V_z \text{ or } +\beta V_{out}$$

$$\text{Therefore } \beta V_z = V_z [1 - (1 + \beta)e^{-T/2\tau}]$$

$$\text{Or } e^{-T/2\tau} = 1 - \beta/1 + \beta$$
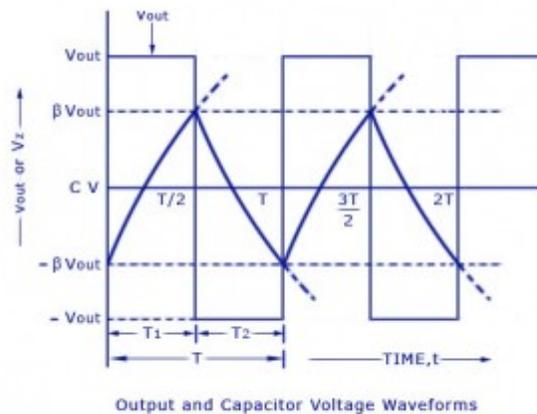
$$\text{Or } T = 2\tau \log_e [1 + \beta/1 - \beta] = 2R_f C \log_e [1 + (2R_3/R_2)]$$



www.CircuitsToday.com

The frequency, $f = 1/T$, of the square-wave is independent of output voltage V_{out} . **This circuit is also known as free-running or astable multivibrator because it has two quasi-stable states.** The output remains in one state for time T_1 and then makes an abrupt transition to the second state and remains in that state for time T_2 . The cycle repeats itself after time $T = (T_1 + T_2)$ where T is the time period of the square-wave.

The op-amp square-wave generator is useful in the frequency range of about 10 Hz -10 kHz. At higher frequencies, the op-amp's slew rate limits the slope of the output square wave. The symmetry of the output waveform depends on the matching of two Zener diodes Z_1 and Z_2 . The unsymmetrical square-wave (T_1 not equal to t_2) can be had by using different constants for charging the capacitor C to $+V_{out}$ and $-V_{out}$