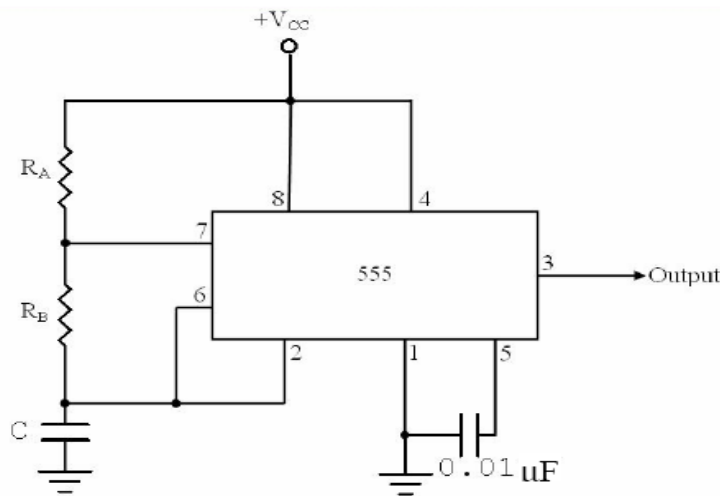



# THE 555 TIMER AS AN ASTABLE MULTIVIBRATOR

An Astable multivibrator, often called a free running multivibrator, is a rectangular wave generating circuit. Unlike the monostable multivibrator, this circuit does not require an external trigger to change the state of the output, hence the name free running. However, the time during which the output is either high or low is determined by 2 resistors and capacitors, which are externally connected to the 555 timer.

**Fig: Astable Multivibrator**



**Model Graph**

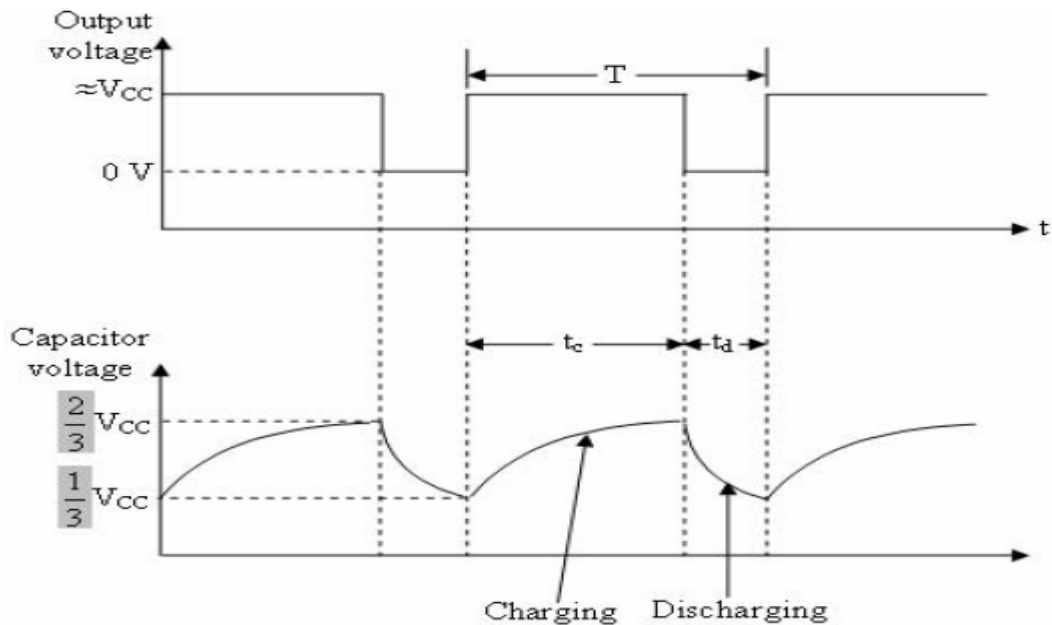

The above figures show the 555 timer connected as an astable multivibrator and its model graph  
**Initially, when the output is high :**

Capacitor C starts charging toward Vcc through RA & RB. However, as soon as voltage across the capacitor equals 2/3 Vcc. Upper comparator triggers the FF & output switches low.

**When the output becomes Low:**

Capacitor C starts discharging through RB and transistor Q1, when the voltage across C equals 1/3 Vcc, lower comparator output triggers the FF & the output goes High. Then cycle repeats. The capacitor is periodically charged & discharged between 2/3 Vcc & 1/3 Vcc respectively. The time during which the capacitor charges from 1/3 Vcc to 2/3 Vcc equal to the time the output is high & is given by

$$t_c = (R_A + R_B)C \ln 2 \dots \dots \dots (1) \text{ Where } [\ln 2 = 0.69]$$

$$= 0.69 (R_A + R_B)C$$

Where RA & RB are in ohms. And C is in farads.

Similarly, the time during which the capacitors discharges from 2/3 Vcc to 1/3 Vcc is equal to the time, the output is low and is given by,

$$t_d = R_B C \ln 2$$

$$t_d = 0.69 R_B C \dots \dots \dots (2)$$

where RB is in ohms and C is in farads.

Thus the total period of the output waveform is

$$T = t_c + t_d = 0.69 (R_A + 2R_B)C \dots \dots \dots (3)$$

This, in turn, gives the frequency of oscillation as,  $f_0 = 1/T = 1.45 / (R_A + 2R_B)C \dots \dots \dots (4)$

Equation 4 indicates that the frequency  $f_0$  is independent of the supply voltage  $V_{cc}$ . Often the term duty cycle is used in conjunction with the astable multivibrator. The duty cycle is the ratio of the time  $t_c$  during which the output is high to the total time period  $T$ . It is generally expressed as a percentage.

$$\% \text{ duty cycle} = (t_c / T) * 100$$

$$\% \text{ DC} = [(R_A + R_B) / (R_A + 2R_B)] * 100$$

### Astable Multivibrator Applications:

#### (a) Square wave oscillator:


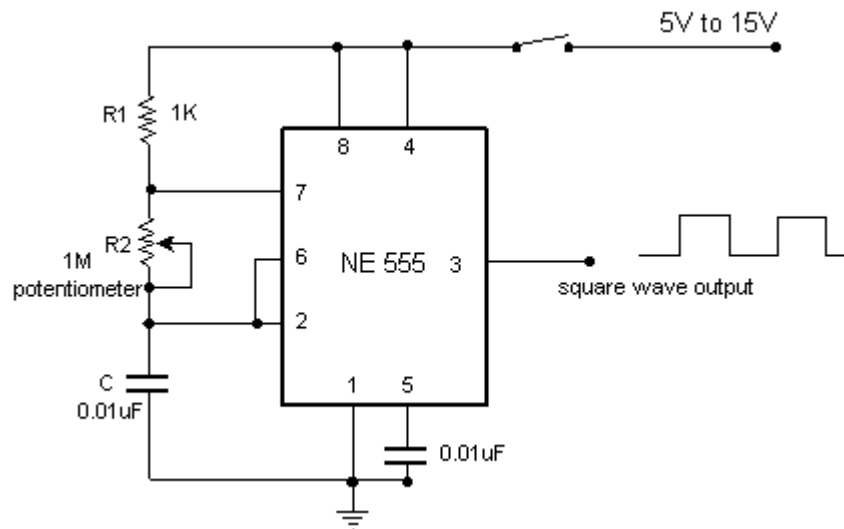


Fig: Square Wave Oscillator

Without reducing  $R_A = 0$  ohm, the astable multivibrator can be used to produce square wave output. Simply by connecting diode  $D$  across Resistor  $R_B$ . The capacitor  $C$  charges through  $R_A$  & diode  $D$  to approximately  $2/3 V_{cc}$  & discharges through  $R_B$  &  $Q1$  until the capacitor voltage equals approximately  $1/3 V_{cc}$ , then the cycle repeats.

To obtain a square wave output,  $R_A$  must be a combination of a fixed resistor & potentiometer so that the potentiometer can be adjusted for the exact square wave.

**(b) Free – running Ramp generator:**

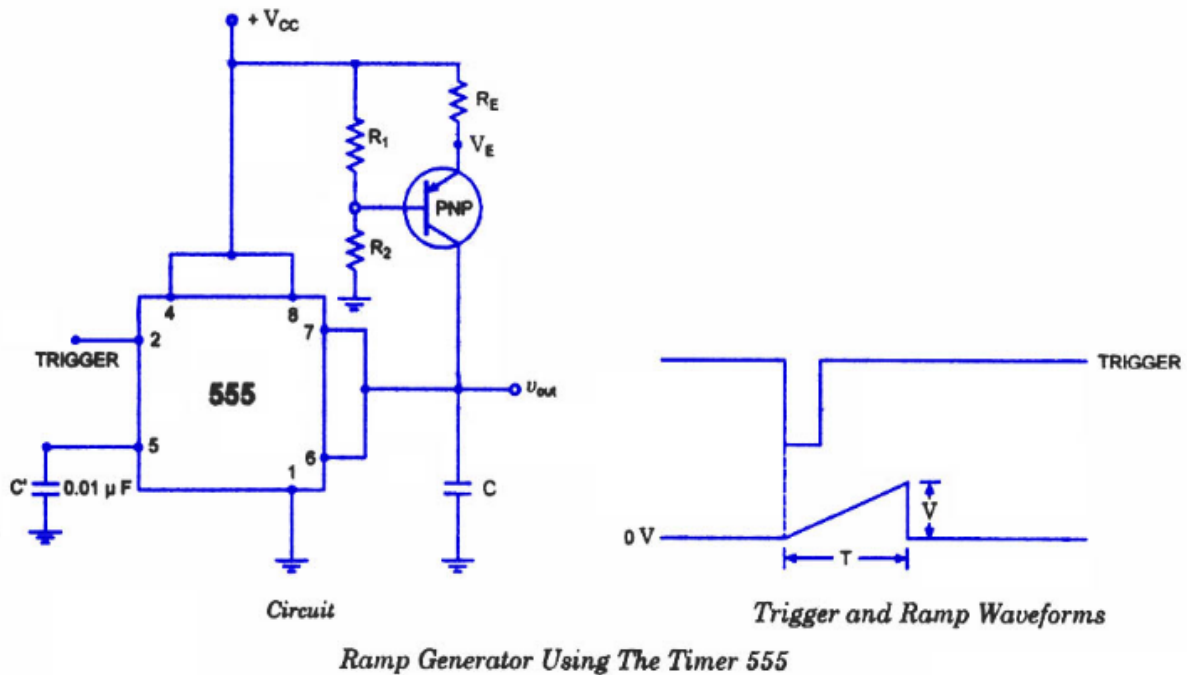

- The astable multivibrator can be used as a free – running ramp generator when resistor  $R_A$  &  $R_B$  are replaced by a current mirror.
- The current mirror starts charging capacitor  $C$  toward  $V_{cc}$  at a constant rate.
- When voltage across  $C$  equals to  $2/3 V_{cc}$ , upper comparator turns transistor  $Q1$  ON &  $C$  rapidly discharges through transistor  $Q1$ .
- When voltage across  $C$  equals to  $1/3 V_{cc}$ , lower comparator switches transistor OFF & then capacitor  $C$  starts charging up again..
- Thus the charge – discharge cycle keeps repeating.
- The discharging time of the capacitor is relatively negligible compared to its charging time.
- The time period of the ramp waveform is equal to the charging time & is approximately is given by,

$$T = V_{cc}C/3I_C \dots\dots\dots (1)$$

$$I_C = (V_{cc} - V_{BE})/R = \text{constant current}$$

Therefore the free – running frequency of ramp generator is

$$f_0 = 3I_C/ V_{cc} C \dots\dots\dots(2)$$