

The Transistor as an Amplifier

The process of linearly increasing the amplitude of an electrical signal is called as Amplification. The signal, $a\beta$ can be defined as anything which carries some relevant information. By using the gain transistor can act as an amplifier. Amplifier is any device which strengthens the amplitude of a signal. The important applications of amplifier are in loud speakers, Bio medical applications etc. When a transistor gets biased in the active (linear) region, the Base-Emitter (BE) junction has a small (Low) resistance due to the forward biasing condition and due to reverse biasing condition; the Base-Collector (BC) junction has a high (Large) resistance.

The Specifications used for the design of transistor as an amplifier are:

i) Consider the DC and AC quantities:

1. Both ac and dc quantities are used in amplifier circuits.
2. For both ac and dc currents capital letters are used.
3. For dc quantities subscript will be capital letter (Uppercase).
4. For ac quantities Subscript will be lowercase (Small letters) .


ii) Transistor Amplification :

, a transistor) β – Since the collector current is equal to the base current multiplied by the current gain (β can amplify the current.

The Base current (I_B) is very small (comparatively very low) compared to I_C and I_E .

– So it is clear that, I_C is almost equal to I_E .

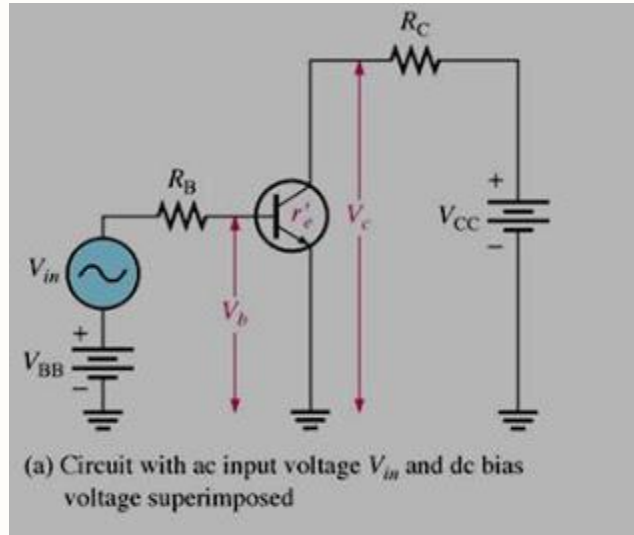Now we can consider the following circuit for the transistor application




– From the circuit, it is clear that at the input side, an ac voltage V_{in} , is superimposed on the applied dc bias voltage V_{BB} .

– Through the collector resistance, R_C , the Dc bias voltage V_{CC} is connected to the collector.

– The ac input voltage can produces an ac base current (at the Base), which will results in a much higher ac collector current than the base current.

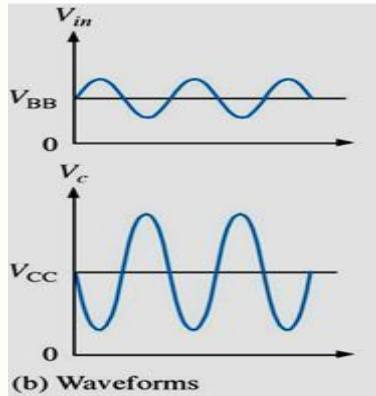– The ac collector current yields to an ac voltage across RC (The collector resistance), will produces an amplified, inverted, reproduction of the ac input voltage in the active region of the transistor.



To the ac wave, the forward biased base-emitter junction present at low resistance. This internal ac emitter resistance can be denoted (represented) by r_e .

$$I_e \text{ (or) } I_c = V_b / r_e$$

$V_c = I_c * R_C$, which is the ac collector voltage,

Since $I_e \approx I_c$, the ac collector voltage can be $V_c \approx I_e R_C$.

$V_b = V_{in} - I_b R_B$, where V_b can be considered as the ac input voltage of the transistor

The transistor ac output voltage can be considered as V_c

– The ratio of V_c to V_b (V_c / V_b) can be defined as the ac voltage gain A_v , of the above transistor circuit.

$$\text{ie, } A_v = V_c / V_b \quad (1)$$

Now we can Substitute $I_e R_C$ for V_c and $I_e r_e$ for V_b which will make (1) as


$$A_v = V_c / V_b \approx (I_e R_C) / (I_e r_e) = R_C / r_e \quad (2)$$

– Thus from (2) it is clear that the amplification depends on the ratio of R_C and r_e .

– R_C will be always much larger in value than r_e , In other words, the output voltage is larger than the input voltage.

Now we can consider one example for the transistor circuit:

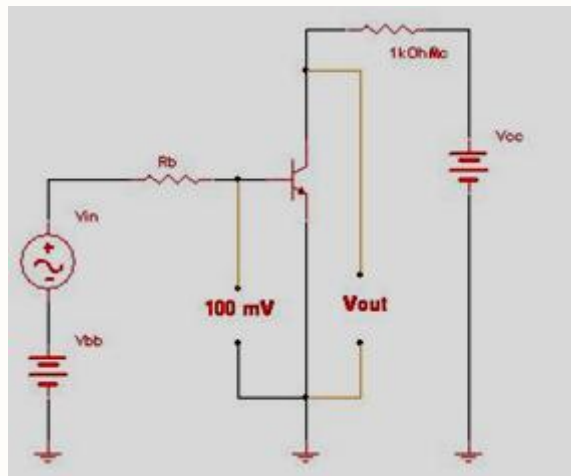Determine the voltage gain and the ac output voltage for the following circuit if $r_e = 120 \Omega$



Solution:

We know that the voltage gain is

$$= 8.333\Omega / 120\Omega \quad A_v ? \quad RC/r'e = 1\text{ k}$$

Hence the output voltage is

$$V_{out} = A_v V_b = (8.333) * (100\text{ mV}) = 0.8333\text{ V}_{rms}$$

Source:

<http://www.electronicandscommunications.com/2013/04/the-transistor-as-amplifier.html>