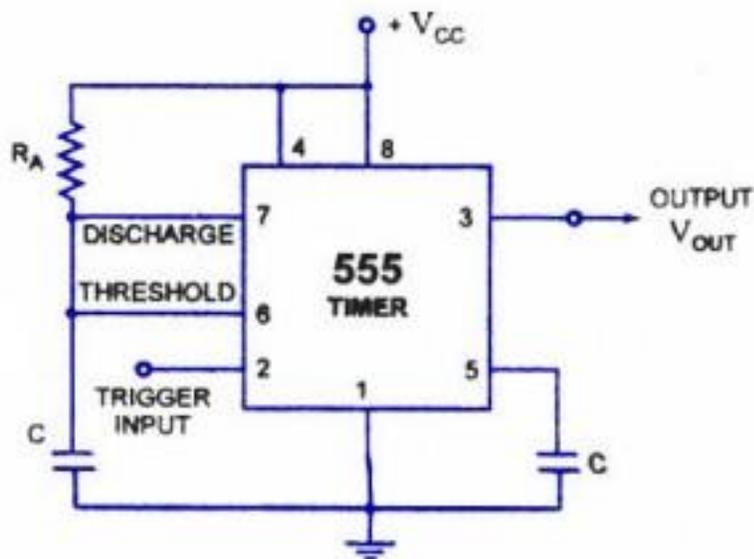


# 555 TIMER AS MONOSTABLE MULTIVIBRATOR

A *monostable multivibrator (MMV) often called a one-shot multivibrator*, is a pulse generator circuit in which the duration of the pulse is determined by the R-C network, connected externally to the **555 timer**. In such a vibrator, one state of output is stable while the other is quasi-stable (unstable). For auto-triggering of output from quasi-stable state to stable state energy is stored by an externally connected capacitor C to a reference level. The time taken in storage determines the pulse width. The transition of output from stable state to quasi-stable state is accomplished by external triggering. The **schematic of a 555 timer** in monostable mode of operation is shown in figure.



*Circuit of The Timer 555  
as a Monostable Multivibrator*


555-timer-monostable-multivibrator

## Monostable Multivibrator Circuit details

Pin 1 is grounded. Trigger input is applied to pin 2. In quiescent condition of output this input is kept at  $+V_{CC}$ . To obtain transition of output from stable state to quasi-stable state, a negative-going pulse of narrow width (a width smaller than expected pulse width of output waveform) and amplitude of greater than  $+2/3 V_{CC}$  is applied to pin 2. Output is taken from pin 3. Pin 4 is usually connected to  $+V_{CC}$  to avoid accidental reset. Pin 5 is grounded through a  $0.01 \mu F$  capacitor to avoid noise problem. Pin 6 (threshold) is shorted to pin 7. A resistor  $R_A$  is connected between pins 6 and 8. At pins 7 a discharge capacitor is connected while pin 8 is connected to supply  $V_{CC}$ .

**555 IC Monostable Multivibrator**

**Operation.**

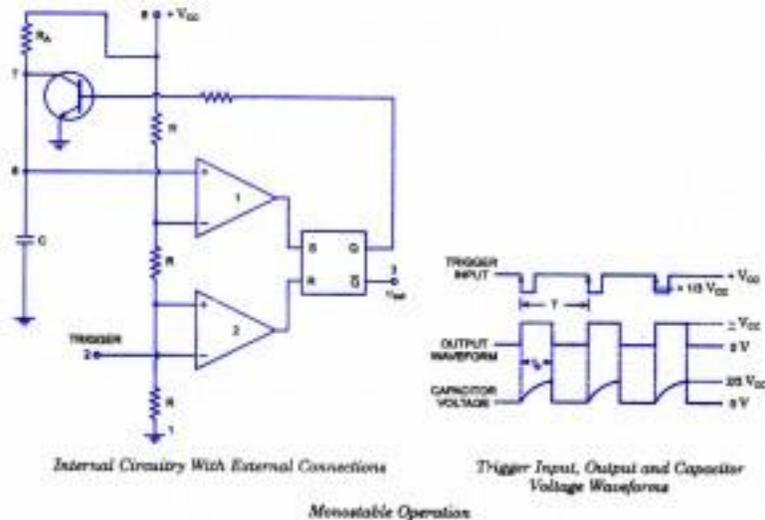

### 555 monostable-multivibrator-operation

For explaining the operation of timer 555 as a monostable **multivibrator**, necessary internal circuitry with external connections are shown in figure.

#### **The operation of the circuit is explained below:**

Initially, when the output at pin 3 is low i.e. the circuit is in a stable state, the transistor is on and capacitor- C is shorted to ground. When a negative pulse is applied to pin 2, the trigger input falls below  $+1/3 V_{CC}$ , the output of comparator goes high which resets the flip-flop and consequently the transistor turns off and the output at pin 3 goes high. This is the transition of the output from stable to quasi-stable state, as shown in figure. As the discharge transistor is cutoff, the capacitor C begins charging toward  $+V_{CC}$  through resistance  $R_A$  with a time constant equal to  $R_A C$ . When the increasing capacitor voltage becomes slightly greater than  $+2/3 V_{CC}$ , the output of comparator 1 goes high, which sets the flip-flop. The transistor goes to saturation, thereby discharging the capacitor C and the output of the timer goes low, as illustrated in figure.

***Thus the output returns back to stable state from quasi-stable state.***

The output of the Monostable Multivibrator remains low until a trigger pulse is again applied. Then the cycle repeats. Trigger input, output voltage and capacitor voltage waveforms are shown in figure.

### **Monostable Multivibrator Design Using 555 timer IC**

The capacitor C has to charge through resistance  $R_A$ . The larger the time constant  $R_A C$ , the longer it takes for the capacitor voltage to reach  $+2/3V_{CC}$ .

In other words, the RC time constant controls the width of the output pulse. The time during which the timer output remains high is given as

$$t_p = 1.0986 R_A C$$

where  $R_A$  is in ohms and C is in farads. The above relation is derived as below. Voltage across the capacitor at any instant during charging period is given as

$$v_c = V_{CC} (1 - e^{-t/R_A C})$$

Substituting  $v_c = 2/3 V_{CC}$  in above equation we get the time taken by the capacitor to charge from 0 to  $+2/3V_{CC}$ .

$$\text{So } +2/3V_{CC} = V_{CC} \cdot (1 - e^{-t/R_A C}) \quad \text{or} \quad t - R_A C \log_e 3 = 1.0986 R_A C$$

$$\text{So pulse width, } t_p = 1.0986 R_A C \approx 1.1 R_A C$$

The pulse width of the circuit may range from micro-seconds to many seconds. This circuit is widely used in industry for many different timing applications.

Source : <http://todayscircuits.blogspot.com/2011/06/555-timer-as-monostable-multivibrator.html#.VUBuwdKqqko>