

INTEGRATOR AND DIFFERENTIATOR

In a differentiator circuit, the output voltage is the differentiation of the input voltage. There are two types of differentiator called passive differentiator and active differentiator. The active differentiator using active components like op-amp.

The output voltage is given by

$$V_{out} = - 1/ (RfCf) [dV_{in} / dt]$$


$$\text{Time constant} = - RfCf$$

The negative sign indicates that there is a phase shift of 180 degree between input and output. The main advantage of such an active differentiator is the small time constant which gives perfect differentiation.

Sometimes a compensation resistance is needed to connect to the non-inverting terminal to provide the bias compensation. The compensation resistance values is given by $R_{comp} = (Rf \text{ parallel with } R1)$.

CIRCUIT DIAGRAM

INTEGRATOR

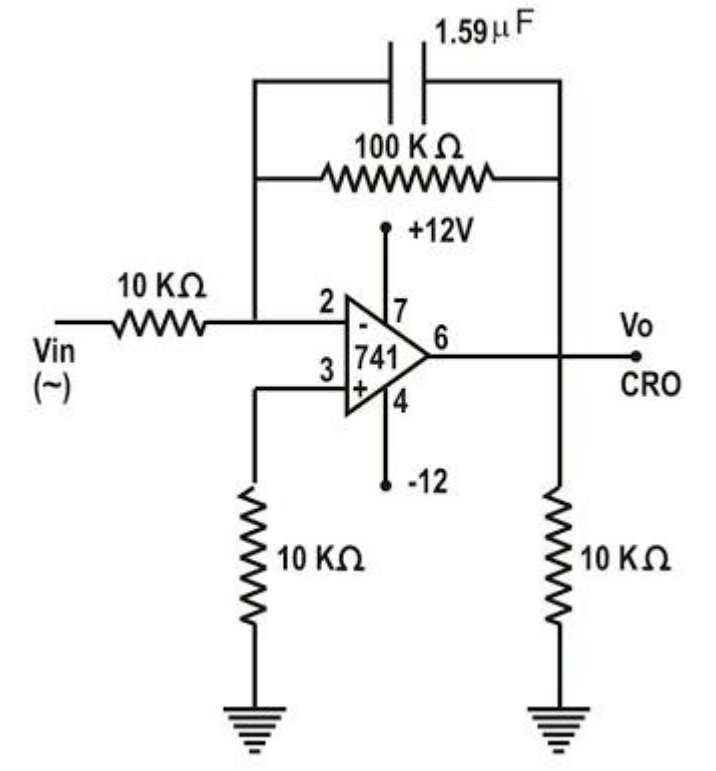

DESIGN

Integrator design

The output voltage is given by

$$V_{out} = - \frac{1}{R_f C_f} \int V_{in}(t) dt + V_o(0)$$

$$\text{Time constant} = R_f C_f$$

1) To find C_f

$$\text{The gain value is given by } A = \frac{R_f}{R_1} \frac{1}{1 + j\omega R_f C_f} \text{-----}$$

---- (1)

The corner frequency is $f_c = 1 / 2\pi R_f C_f$ -----

--- - (2)

Choose, $f_c = 100\text{Hz}$ and

$R_f = 10\text{K}\Omega$

By substituting all in equation (2), calculate the value of C_f .


2) To find R_1

Let Gain (A) = 1 and substitute all remaining values in equation (1),

then find the value of R_1 .


MODEL GRAPH

INTEGRATOR

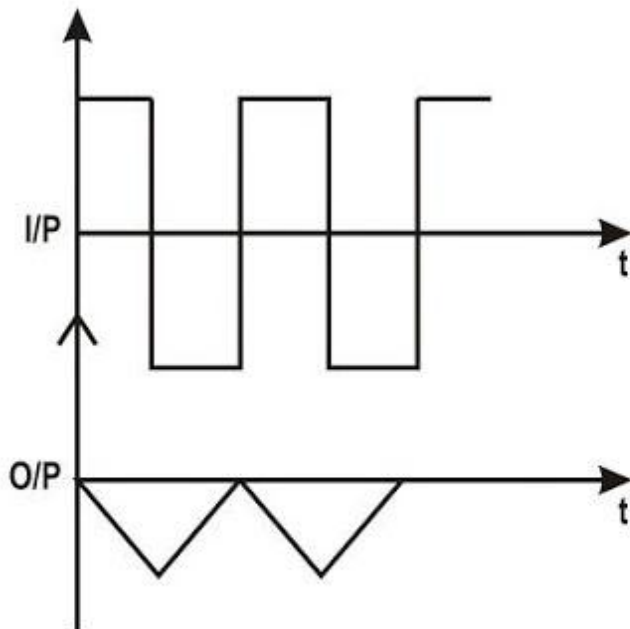

CIRCUIT DIAGRAM

DIFFERENTIATOR

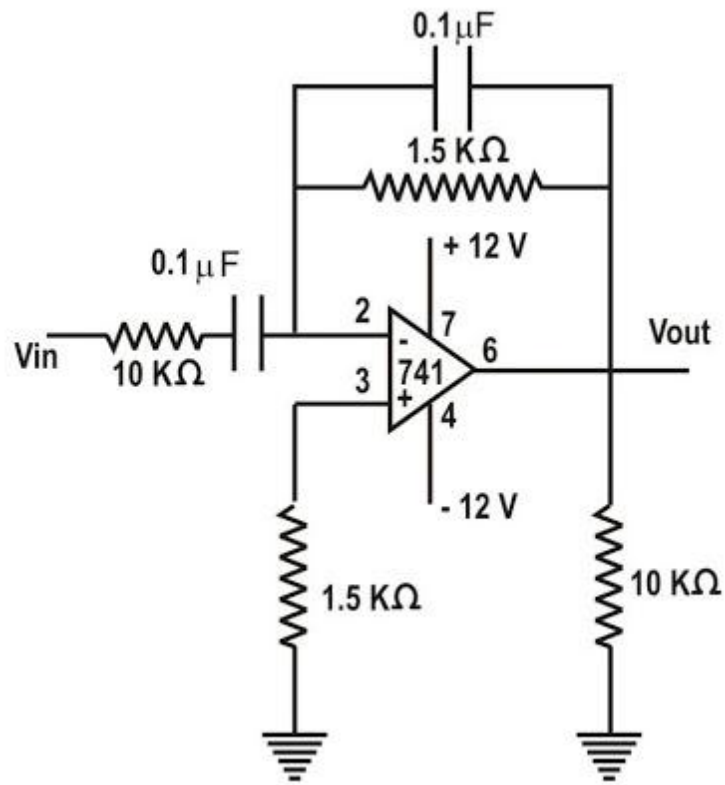

DESIGN

Differentiator design

The gain value is given by $A = -j\omega R_f C_1 / (1 + j\omega R_1 C_1)^2$ -----

----- (1)

The lower corner frequency is $f_a = 1 / 2\pi R_1 C_1$ -----

----- (2)

The upper corner frequency is $f_b = 1 / 2\pi R_f C_1$ -----

----- (3)

Always assume $f_a < f_b < f_c$ and $R_f C_1 < T$. Where T is time constant.

Design procedure

1. Choose f_a as the highest frequency of the input signal. i.e. $f_a = 100\text{Hz}$
2. Choose C_1 to be less than 1 micro Farad and calculate the value of R_1 .


Choose $C = 1\text{micro Farad}$ and from equation (2) and Calculate R_1 .

3. Choose f_b as 10 times f_a which ensures that $f_a < f_b$. That is $f_b = 10 f_a$. Now find R_f .

4. To find C_f , use $R_f C_1 = R_1 C_1$ and $R_{\text{comp}} = R_1$ parallel with R_f .

MODEL GRAPH

DIFFERENTIATOR

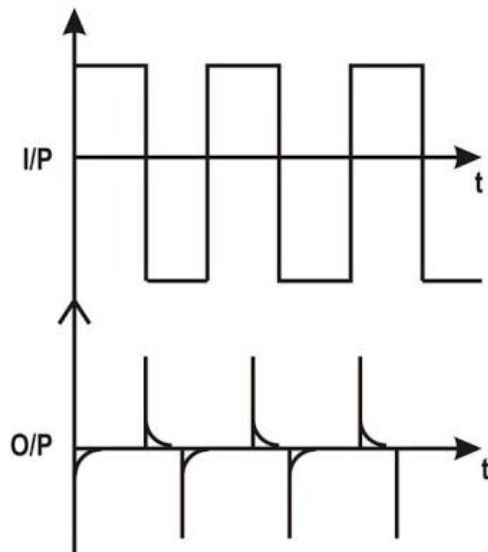

Source: <http://mediatoget.blogspot.in/2012/01/integrator-and-differentiator.html>