

PHASE LOCKED LOOPS (PLL)

Introduction to PLL


The concept of Phase Locked Loops (PLL) first emerged in the early 1930's. But the technology was not developed as it now, the cost factor for developing this technology was very high. Since the advancement in the field of integrated circuits, PLL has become one of the main building blocks in the electronics technology. In present, the PLL is available as a single IC in the SE/NE560 series (560, 561, 562, 564, 565 and 567) to further reduce the buying cost, the discrete IC's are used to construct a PLL.

PLL Applications

- ☐ Frequency Modulation (FM) stereo decoders, FM Demodulation networks for FM operation.
- ☐ Frequency synthesis that provides multiple of a reference signal frequency.
- ☐ Used in motorspeed controls, tracking filters.
- ☐ Used in frequency shift keying (FSK) decodes for demodulation carrier frequencies.

PLL Block Diagram

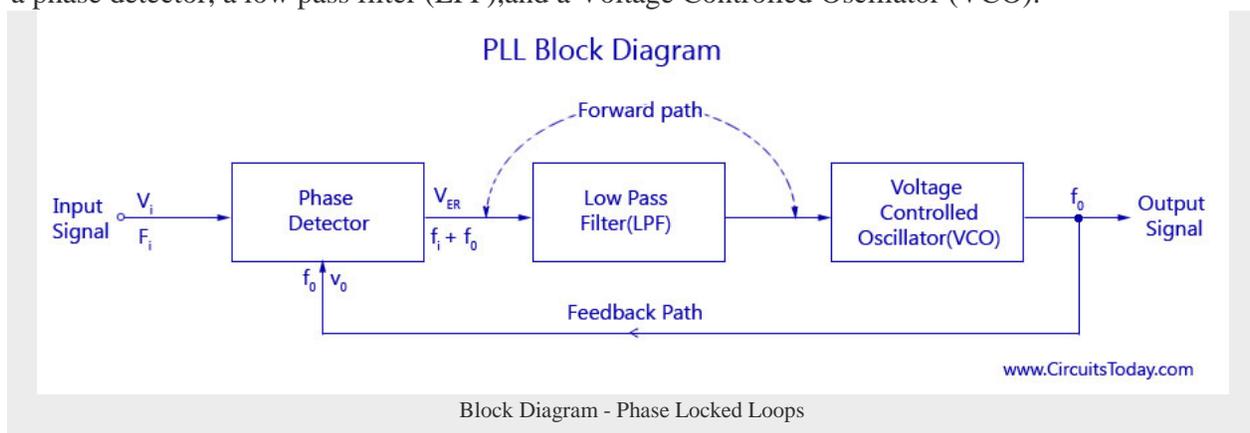The block diagram of a basic PLL is shown in the figure below. It is basically a flip flop consisting of a phase detector, a low pass filter (LPF), and a Voltage Controlled Oscillator (VCO).



Block Diagram - Phase Locked Loops

The input signal V_i with an input frequency f_i is passed through a phase detector. A phase detector basically a comparator which compares the input frequency f_i with the feedback frequency f_o . The phase detector provides an output error voltage V_{ER} ($=f_i + f_o$), which is a DC voltage. This DC voltage is then passed on to an LPF. The LPF removes the high frequency noise and produces a steady DC level, V_f ($=f_i - f_o$). V_f also represents the dynamic characteristics of the PLL.

The DC level is then passed on to a VCO. The output frequency of the VCO (f_o) is directly proportional to the input signal. Both the input frequency and output frequency are compared and

adjusted through feedback loops until the output frequency equals the input frequency. Thus the PLL works in these stages – free-running, capture and phase lock.

As the name suggests, the free running stage refer to the stage when there is no input voltage applied. As soon as the input frequency is applied the VCO starts to change and begin producing an output frequency for comparison this stage is called the capture stage. The frequency comparison stops as soon as the output frequency is adjusted to become equal to the input frequency. This stage is called the phase locked state.


Now let us study in detail about the various parts of a PLL – The phase detector, Low Pass Filter and Voltage Controlled Oscillator.

1. Phase Detector

This comparator circuit compares the input frequency and the VCO output frequency and produces a dc voltage that is proportional to the phase difference between the two frequencies. The phase detector used in PLL may be of analog or digital type. Even though most of the monolithic PLL integrated circuits use analog phase detectors, the majority of discrete phase detectors are of the digital type. One of the most commonly used analog phase detector is the double balanced mixer circuit. Some of the common digital type phase detectors are

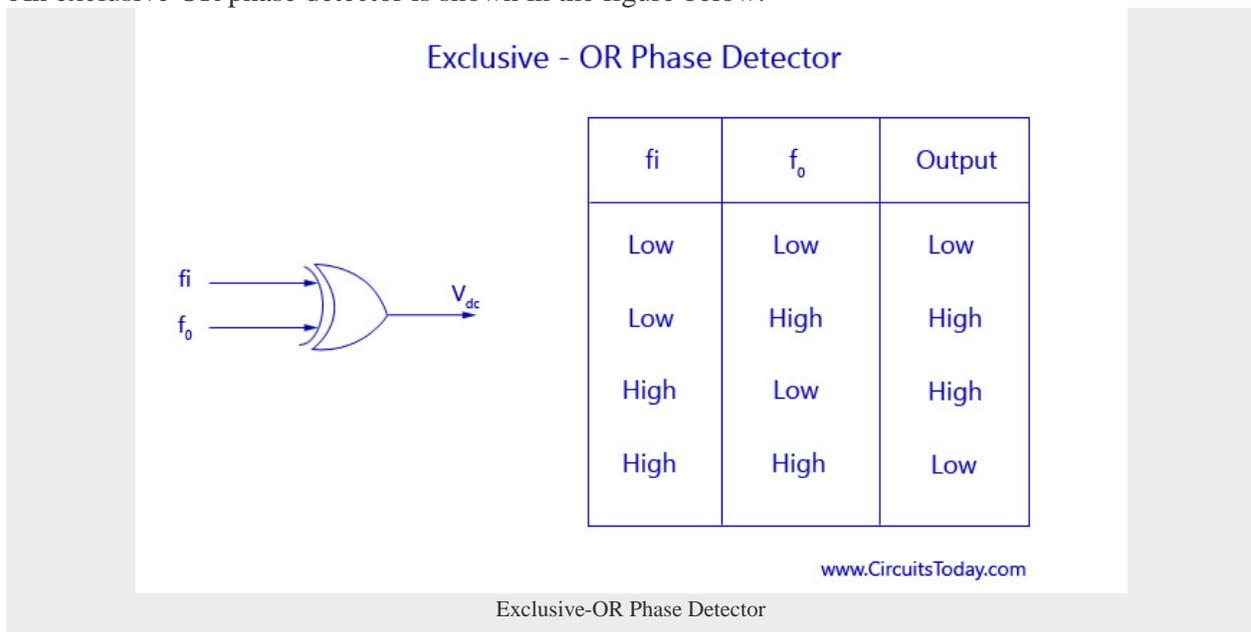1.1 Exclusive OR Phase Detector


An exclusive OR phase detector is shown in the figure below.



It is obtained as a CMOS IC of type 4070. Both the frequencies are provided as an input to the EX OR phase detector. Obeying the EX-OR concept the output becomes HIGH only if either of the inputs f_i or f_o becomes HIGH. All other conditions will produce a LOW output. Let us consider a waveform where the input frequency leads the output frequency by θ degrees. That is, f_i and f_o has a

phase difference of θ degrees. The dc output voltage of the comparator will be a function of the phase difference between its two inputs.

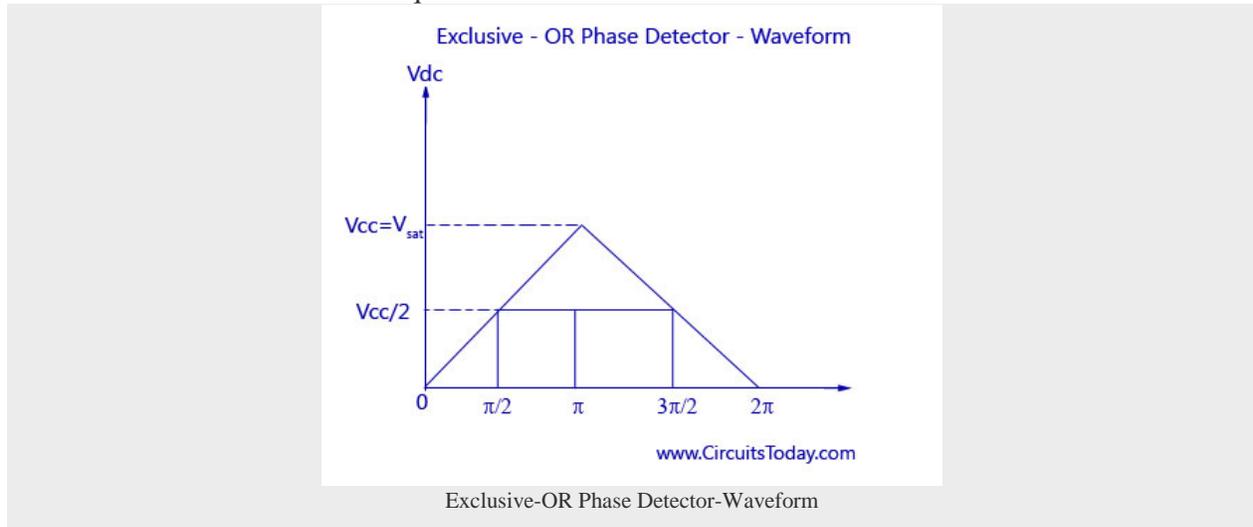The figure shows the graph of DC output voltage as a function of the phase difference between f_i and f_o . The output DC voltage is maximum when the phase detector is 180° . This type of phase detector is used when both f_i and f_o are square waves.



1.2 Edge Triggered Phase Detector

Edge triggered phase detector is used when f_i and f_o are pulse waveforms with less than 50% duty cycles. The figure of such a phase detector using an R-S Flip Flop is shown below. Two NOR Gate (CD4001) are cross-coupled to form an R-S Flip Flop. The output of the phase detector changes its logic state by triggering of the R-S Flip Flop. That is, the output of the phase detector changes its logic state on the positive edge of the input f_i and f_o . The advantage of such a detector can be understood from the graph below. It is clear that the DC output voltage is linear over 360° .

1.3 Monolithic Phase Detectors

The monolithic type phase detector uses a CMOS type 4044 IC, which is highly advantageous as the harmonic sensitivity and duty cycle problems are neglected and the circuit will respond only to the transition in the input signals. This is the most preferred phase detector in the critical applications as the phase error and the output error voltage are independent of variations in the amplitude and duty cycles of the input waveforms.

2. Low Pass Filter (LPF)

A Low Pass Filter (LPF) is used in Phase Locked Loops (PLL) to get rid of the high frequency components in the output of the phase detector. It also removes the high frequency noise. All these features make the LPF a critical part in PLL and help control the dynamic characteristics of the whole circuit. The dynamic characteristics include capture and lock ranges, bandwidth, and transient response. The lock range is the tracking range where the range of frequencies of the PLL system

follows the changes in the input frequency. The capture range is the range in which the Phase Locked Loops attains the Phase Lock.

When the filter bandwidth is reduced, the response time increases. But this reduces the capture range. But it also helps in reducing noise and in maintaining the locked loop through momentary losses of signal. Two types of passive filter are used for the LPF circuit in a PLL. An amplifier is used also with LPF to obtain gain. The active filter used in PLL is shown below.

3. Voltage Controlled Oscillator (VCO)

The main function of the VCO is to generate an output frequency that is directly proportional to the input voltage. The connection diagram of a SE/NE 566 VCO is shown in the figure below. The maximum frequency of the VCO is 500 KHz.

This VCO provides simultaneous square wave and triangular wave outputs as a function of the input voltage. The frequency of oscillation is determined by the resistor R and capacitor C along with the voltage V_c applied to the control terminal.

Source : <http://www.circuitstoday.com/pll-phase-locked-loops#PLL-Working>