

SINGLE PHASE BRIDGE INVERTER WITH RL LOAD

The operation of the circuit can be divided into four intervals or modes. The waveforms are as shown in Fig. 8.13.

Interval I ($t_1 - t_2$):

At instant t_1 , the pair of transistors Q_1 and Q_2 is turned on. The transistors are assumed to be ideal switches. Therefore point A gets connected to positive point of dc source V through Q_1 , and point B gets connected to negative point of input supply.

The output voltage $V_o = +V$ as shown in Fig 8.11(a). The load current starts increasing exponentially due to the inductive nature of the load.

The instantaneous current through Q_1 and Q_2 is equal to the instantaneous load current. The energy is stored into the inductive load during this interval of operation.

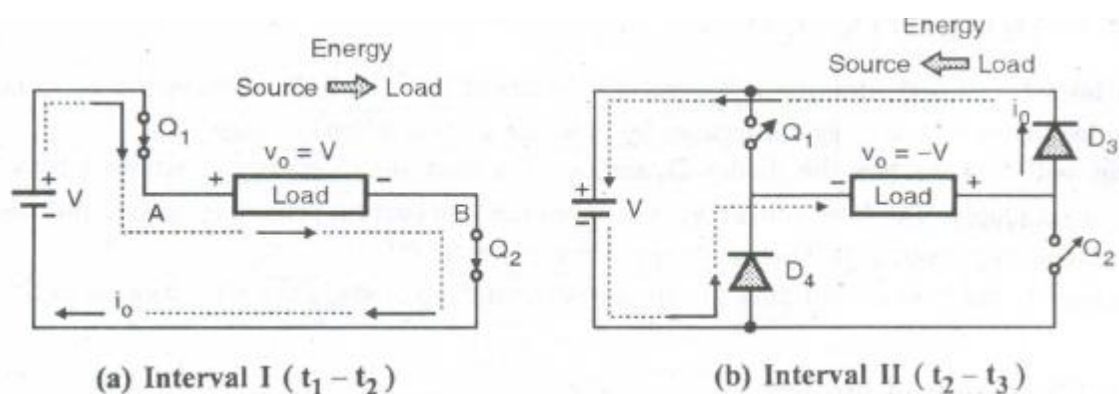


Fig.8.11

Interval II ($t_2 - t_3$):

- At instant t_2 both the transistors Q_1 and Q_2 are turned off. But the load current does not reduce to 0 instantaneously, due to its inductive nature.
- So in order to maintain the flow of current in the same direction there is a self induced voltage across the load. The polarity of this voltage is exactly opposite to that in the previous mode.
- Thus output voltage becomes negative equal to $-V$. But the load current continues to now in the same direction, through D_3 and D_4 as shown in Fig. 8.11(b).
- Thus the stored energy in the load inductance is returned back to the source in this mode. The diodes D_1 to D_4 are therefore known as the feedback diodes.
- The load current decreases exponentially and goes to 0 at instant t_3 when all the energy stored in the load is returned back to supply. D_3 and D_4 are turned off at t_3 .

Interval III ($t_3 - t_4$)

- At instant t_3 Q_3 and Q_4 are turned on simultaneously. The load voltage remains negative equal to $-V$ but the direction of load current will reverse and become negative.
- The current increases exponentially in the negative direction. And the load again stores energy in this mode of operation. This is as shown in Fig. 8.12(a).

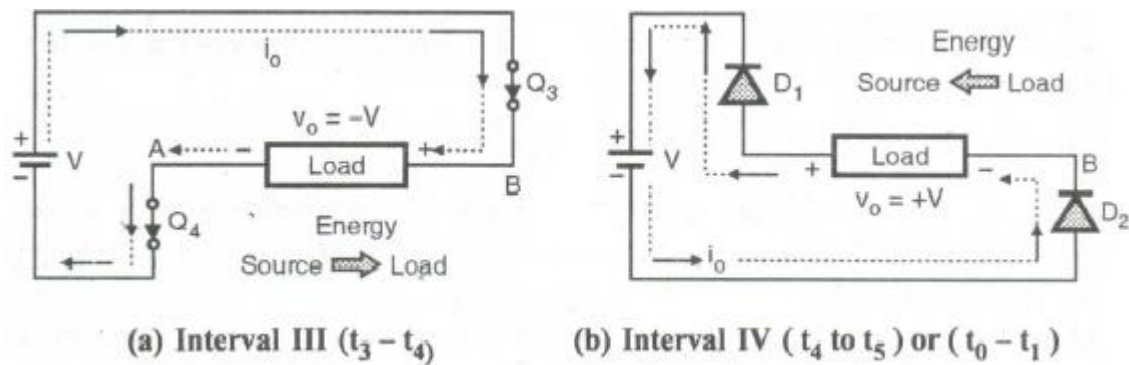


Fig.8.12

Interval IV (t_4 to t_5) or (t_0 to t_1)

- At instant t_4 or to the transistors Q_3 and Q_4 are turned off. The load inductance tries to maintain the load current in the same direction, by inducing a positive load voltage.
- This will forward bias the diodes D_1 and D_2 . The load stored energy is returned back to the input dc supply. The load voltage $V_o = +V$ but the load current remains negative and decrease exponentially towards 0. This is as shown in Fig. 8.12(b).
- At t_5 or t_1 the load current goes to zero and transistors Q_1 and Q_2 can be turned on again.

Conduction period of devices:

- The conduction period with a very highly inductive load, will be $T/4$ or 90° for all the transistors as well as the diodes.
- The conduction period of transistors will increase towards $T/2$. or 180° with increase in the load power factor. (i.e., as the load becomes more and more resistive).

Source : <http://elearningatria.files.wordpress.com/2013/10/ece-vii-power-electronics-10ec73-notes.pdf>