
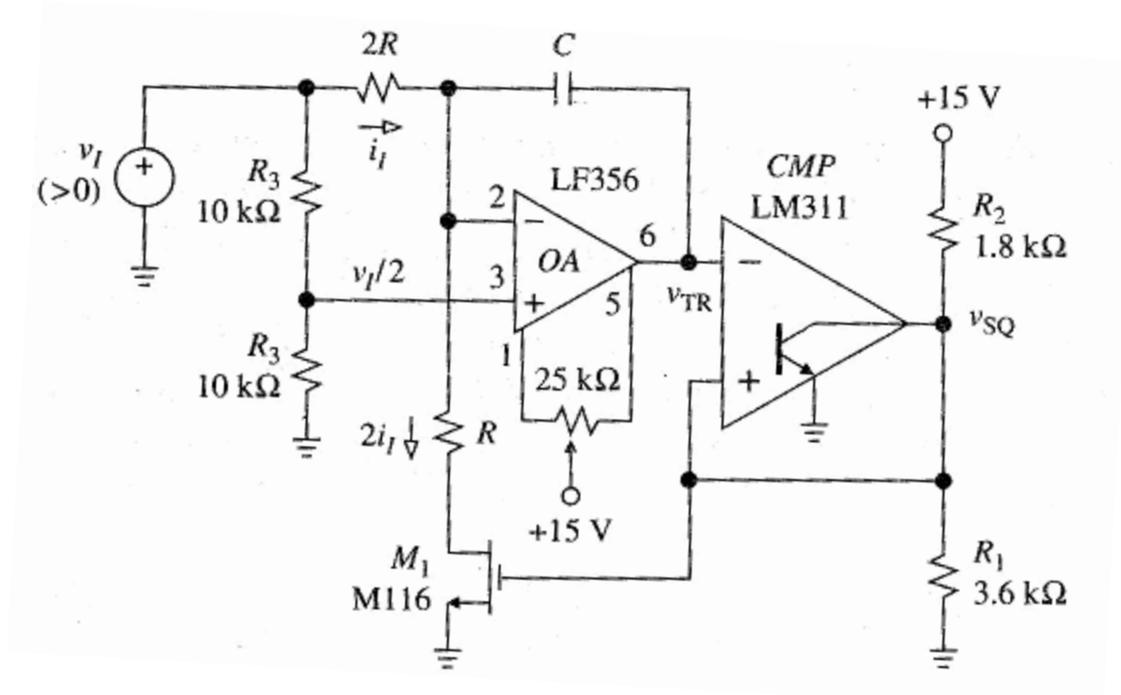


TRIANGULAR WAVE GENERATOR

Circuit:

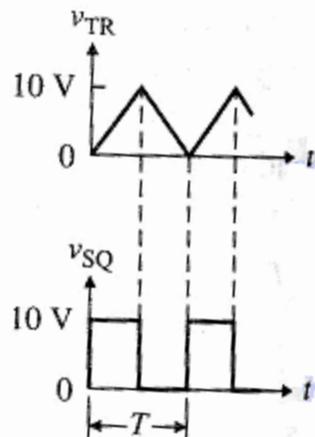


This signal generator gives you two waveforms for the price of one: a triangle-wave and a square-wave. The central component of this circuit is the integrator capacitor C . Basically we are interested in performing two functions on C : *charge it, discharge it - repeat indefinitely*. The output waveforms are shown here and it is apparent that a square wave generator followed by an integrator acts as a triangular wave generator.



Suppose our design calls for a +/-10 V triangle wave, cruising along at 10 kHz. This means that $V_{th+} = +10$ V and $V_{th-} = -10$ V. Given $V_P = +5$ V, $V_N = -5$ V, let's choose $R_2 = 10$ k Ω and then calculate $R_1 = 20$ k Ω from the equation above. If the value of Capacitor is 1 nf, then what value of R_1 is needed for 10 kHz ($T = 100$ μ s) can be calculated, because V_o needs to swing $\Delta V_o = 10 - (-10) = 20$ V in an interval $\Delta T = 50$ μ s, we solve the above equation in the Linear Ramps section for R_1 .

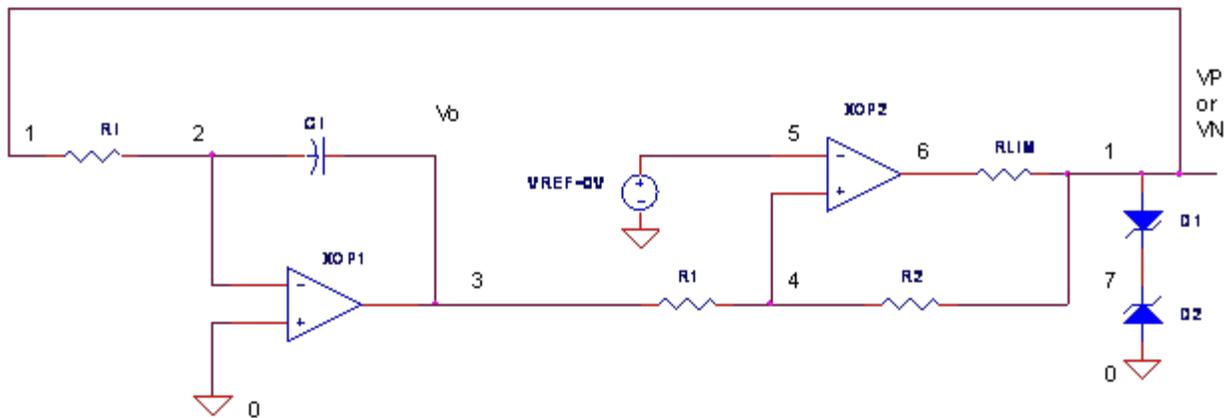Changing the voltage thresholds also changes the time required to reach the thresholds. Also, make sure V_{th+} and V_{th-} are not outside the +/-15V limits of the op amp model. And don't forget the option of changing the reverse voltage of the zener diode via the BV parameter. Just remember the charging currents and thresholds will change too.



You may have noticed that the triangle peaks and period may not accurately meet our +/-10V swing at 100 μ s. The main reason is that our current source and thresholds are derived from zener diodes - not exactly the most accurate reference. Some designs use improved means for deriving and switching the current sources that charge CI.